



Gowin HDL Coding User Guide

SUG949-2.1E, 12/31/2025

Copyright © 2025 Guangdong Gowin Semiconductor Corporation. All Rights Reserved.

GOWIN and LittleBee are trademarks of Guangdong Gowin Semiconductor Corporation and are registered in China, the U.S. Patent and Trademark Office, and other countries. All other words and logos identified as trademarks or service marks are the property of their respective holders. No part of this document may be reproduced or transmitted in any form or by any means, electronic, mechanical, photocopying, recording or otherwise, without the prior written consent of GOWINSEMI.

Disclaimer

GOWINSEMI assumes no liability and provides no warranty (either expressed or implied) and is not responsible for any damage incurred to your hardware, software, data, or property resulting from usage of the materials or intellectual property except as outlined in the GOWINSEMI Terms and Conditions of Sale. GOWINSEMI may make changes to this document at any time without prior notice. Anyone relying on this documentation should contact GOWINSEMI for the current documentation and errata.

Revision History

Date	Version	Description
08/31/2020	1.0E	Initial version published.
06/10/2021	1.1E	Infer case of single-ended BUF added.
05/31/2022	1.2E	The description of Guideline on HDL Coding removed.
04/30/2025	1.8E	● VHDL examples added. ● Decoder form of SP removed.
08/29/2025	2.0E	● Chapter 2 Introduction updated. ● Chapter 3 Registers updated. ● Chapter 4 Latches updated. ● Chapter 5 Tristate Buffers updated. ● Chapter 6 Bidirectional Buffers updated. ● Chapter 7 Shift Registers updated. ● Chapter 8 RAM updated. ● Chapter 9 ROM updated. ● Chapter 10 DSP updated. ● Chapter 11 FSM updated.
12/31/2025	2.1E	Updated entity names in some VHDL examples.

Contents

Contents	i
List of Tables.....	iv
1 About This Guide	1
1.1 Purpose	1
1.2 Related Documents	1
1.3 Terminology and Abbreviations.....	2
1.4 Support and Feedback	2
2 Introduction	3
3 Registers.....	4
3.1 Registers Recognized by GowinSynthesis.....	4
3.2 Coding Guidelines	4
3.3 Register Examples.....	4
3.3.1 Register with Clock Enable and Synchronous Set (Verilog).....	4
3.3.2 Register with Clock Enable and Synchronous Set (VHDL)	5
3.3.3 Register with Clock Enable and Synchronous Reset (Verilog).....	6
3.3.4 Register with Clock Enable and Synchronous Reset (VHDL)	6
3.3.5 Register with Clock Enable and Asynchronous Preset (Verilog).....	7
3.3.6 Register with Clock Enable and Asynchronous Preset (VHDL)	7
3.3.7 Register with Clock Enable and Asynchronous Clear (Verilog).....	8
3.3.8 Register with Clock Enable and Asynchronous Clear (VHDL)	9
4 Latches	11
4.1 Latches	11
4.2 Latch Examples	11
4.2.1 Data Latch with Asynchronous Clear and Latch Enable (Verilog).....	11
4.2.2 Data Latch with Asynchronous Preset and Latch Enable (Verilog)	12
4.2.3 Data Latch with Asynchronous Preset and Latch Enable (VHDL)	12
5 Tristate Buffers.....	14
5.1 Tristate Buffers.....	14
5.2 Tristate Buffer Examples	14

5.2.1 TriState Using Concurrent Assignment (Verilog)	14
5.2.2 TriState Using Concurrent Assignment (VHDL)	14
5.2.3 Tristate Using Combinatorial Logic (Verilog)	15
5.2.4 Tristate Using Combinatorial Logic (VHDL)	15
6 Bidirectional Buffers	17
6.1 Bidirectional Buffers	17
6.2 Bidirectional Buffer Examples	17
6.2.1 Bidirectional Using Concurrent Assignment (Verilog)	17
6.2.2 Bidirectional Using Concurrent Assignment (VHDL)	17
6.2.3 Bidirectional Using Combinatorial Logic (Verilog)	18
6.2.4 Bidirectional Using Combinatorial Logic (VHDL)	18
7 Shift Registers	20
7.1 Static Shift Registers	20
7.1.1 Static Shift Registers	20
7.1.2 Static Shift Register Examples	20
7.2 Dynamic Shift Registers	23
7.2.1 Dynamic Shift Registers	23
7.2.2 Dynamic Shift Register Examples	23
8 RAM	28
8.1 BSRAM	28
8.1.1 Single-Port BSRAM Examples	28
8.1.2 Semi Dual-Port BSRAM Examples	37
8.1.3 Dual-Port BSRAM Examples	49
8.1.4 Byte-enable	59
8.2 SSRAM	74
8.2.1 Single-Port SSRAM with Synchronous Read Examples	74
8.2.2 Semi Dual-Port SSRAM with Synchronous Read Examples	76
8.3 RAM Initialization	78
8.3.1 Specifying RAM Initialization in HDL Source Code	78
8.3.2 Specifying RAM Initialization Content in External Data Files	81
9 ROM	88
9.1 ROM Examples	88
9.1.1 ROM with Initial Values Assigned at Definition (Verilog)	88
9.1.2 ROM with Initial Values Assigned at Definition (VHDL)	89
9.1.3 ROM Implemented Using Case Statement (Verilog)	91
9.1.4 ROM Implemented Using Case Statement (VHDL)	94
9.1.5 ROM with Initial Values Assigned Using Initial Block (Verilog)	97
9.1.6 ROM with Initial Values Assigned Using readmemh (Verilog)	98

9.1.7 ROM with Initial Values Assigned Using readmemb (Verilog)	100
9.1.8 ROM with Initial Values Assigned Using readline (VHDL)	103
10 DSP	107
10.1 Pre-adder	107
10.1.1 Static Pre-adder/subtractor Operation Examples	107
10.1.2 Dynamic Pre-adder/subtractor Operation Examples	113
10.2 Multiplier	121
10.2.1 Multiplier Examples.....	121
10.3 Multiply-Accumulator (MAC).....	127
10.3.1 Static Multiply-add/subtract Examples.....	127
10.3.2 Dynamic Multiply-add/subtract Examples.....	134
10.4 Accumulator	142
10.4.1 Static Accumulator Examples	142
10.4.2 Dynamic Accumulator Examples	150
10.5 Cascadeing.....	159
10.5.1 Static Cascadeing Examples.....	159
10.5.2 Dynamic Cascadeing Examples	167
10.6 Shifting.....	176
10.6.1 Shifting Examples	176
10.7 Arithmetic Logic Operation	180
10.7.1 Arithmetic Logic Examples	180
11 FSM	183
11.1 FSM Description	183
11.2 Encoding Schemes.....	183
11.3 FSM Examples.....	183
11.3.1 Moore FSM with One-hot Encoding (Verilog)	183
11.3.2 Moore FSM with One-hot Encoding (VHDL).....	186
11.3.3 Mealy FSM with One-hot Encoding (Verilog).....	188
11.3.4 Mealy FSM with One-hot Encoding (VHDL)	191
11.3.5 Moore FSM with Gray Code Encoding (Verilog).....	193
11.3.6 Moore FSM with Gray Code Encoding (VHDL)	196
11.3.7 Mealy FSM with Gray Code Encoding (Verilog)	198
11.3.8 Mealy FSM with Gray Code Encoding (VHDL).....	201
11.3.9 Moore FSM with Sequential Encoding (Verilog)	203
11.3.10 Moore FSM with Sequential Encoding (VHDL).....	206
11.3.11 Mealy FSM with Sequential Encoding (Verilog)	208
11.3.12 Mealy FSM with Sequential Encoding (VHDL)	211

List of Tables

Table 1-1 Abbreviations and Terminology	2
---	---

1 About This Guide

1.1 Purpose

This manual describes the guideline on Gowin HDL coding and its primitive implementation, and It is intended to help users quickly become familiar with Gowin HDL coding to improve design efficiency.

1.2 Related Documents

The latest user guides are available on GOWINSEMI Website. You can find the related documents at www.gowinsemi.com:

- [SUG100, Gowin Software User Guide](#)
- [SUG283, Gowin Primitive User Guide](#)
- [UG285, Gowin BSRAM & SSRAM User Guide](#)
- [UG287, Gowin Digital Signal Processing \(DSP\) User Guide](#)
- [UG288, Gowin Configurable Function Unit \(CFU\) User Guide](#)
- [UG289, Gowin Programmable IO \(GPIO\) User Guide](#)
- [UG300, Arora V BSRAM & SSRAM User Guide](#)
- [UG303, Arora V Configurable Function Unit \(CFU\) User Guide](#)
- [UG304, Arora V Programmable IO \(GPIO\) User Guide](#)
- [UG305, Arora V Digital Signal Processing \(DSP\) User Guide](#)

1.3 Terminology and Abbreviations

Table 1-1 shows the abbreviations and terminology used in this manual.

Table 1-1 Abbreviations and Terminology

Terminology and Abbreviations	Meaning
BSRAM	Block Static Random Access Memory
CLU	Configurable Logic Unit
DSP	Digital Signal Processing
FSM	Finite State Machine
HDL	Hardware Description Language
LUT	Look-up Table
SSRAM	Shadow Static Random Access Memory

1.4 Support and Feedback

Gowin Semiconductor provides customers with comprehensive technical support. If you have any questions, comments, or suggestions, please feel free to contact us directly by the following ways.

Website: www.gowinsemi.com

E-mail: support@gowinsemi.com

2 Introduction

HDL coding is a core methodology in digital logic design, enabling precise description of circuit behavior and structure, and efficient mapping to the hardware resources of the target device. This guide will help users to:

- Implement common digital logic functions

Describe combinational logic (e.g., lookup tables, multiplexers), sequential logic (e.g., registers), and complex state machines. Synthesizable RTL templates are provided to avoid inconsistencies between simulation and hardware implementation.

- Adapt to Gowin device architectures

Apply optimized coding methods for device-specific resources such as Block RAM and DSP units.

Through standardized HDL design, developers can fully leverage the performance and power efficiency advantages of Gowin FPGAs while reducing debugging risks in later stages. For general requirements of Gowin HDL coding, refer to Chapter 2 in [SUG113, Gowin FPGA Design User Guide](#).

This document includes coding examples and supports downloading the corresponding example files.

3 Registers

3.1 Registers Recognized by GowinSynthesis

GowinSynthesis can recognize registers with the following control signals:

- Rising-edge or falling-edge clock
- Asynchronous set/reset
- Synchronous set/reset
- Clock enable

3.2 Coding Guidelines

1. When declaring a register, an initial value must be assigned.
2. Do not code registers that include both set and reset functions at the same time.
3. If a register has an initial value, its set/reset value must be consistent with the initial value.
4. Use non-blocking assignments to describe registers.
5. A sequential logic circuit must not have more than two signals in its sensitivity list.

3.3 Register Examples

3.3.1 Register with Clock Enable and Synchronous Set (Verilog)

```
// 1-bit Register with Rising-edge Clock
// Active-high Synchronous Set
// Active-high Clock Enable
module gowin_dffse (clk, d, ce, set, q );
input clk, d, ce, set;
output reg q=1'b1;
always @(posedge clk)begin
```

```

        if (set)begin
            q <= 1'b1;
        end
        else begin
            if (ce)begin
                q <= d;
            end
        end
    end
end
endmodule

```

3.3.2 Register with Clock Enable and Synchronous Set (VHDL)

```

-- 1-bit Register with Rising-edge Clock
-- Active-high Synchronous Set
-- Active-high Clock Enable
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity gowin_dffse IS
    PORT(q:OUT std_logic;
          d :IN  std_logic;
          set:IN  std_logic;
          ce:IN  std_logic;
          clk:IN std_logic
    );
end gowin_dffse;
ARCHITECTURE rtl OF gowin_dffse IS
begin
    process(clk)
    begin
        if(clk 'event and clk ='1') then
            if(set='1')then
                q<='1';
            elsif(ce='1')then
                q<=d;
            end if;
        end if;
    end process;
end rtl;

```

```

        end if;
    end process;
end;
```

3.3.3 Register with Clock Enable and Synchronous Reset (Verilog)

```

// 1-bit rising-edge clock register
// Active-high synchronous reset
// Active-high clock enable
module gowin_dffre (clk, d, ce, rst, q );
input clk, d, ce, rst;
output reg q= 1'b0;
always @(posedge clk)begin
    if (rst)begin
        q <= 1'b0;
    end
    else begin
        if (ce)begin
            q <= d;
        end
    end
end
endmodule
```

3.3.4 Register with Clock Enable and Synchronous Reset (VHDL)

```

-- 1-bit rising-edge clock register
-- Active-high synchronous reset
-- Active-high clock enable
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity gowin_dffre IS
    PORT(q:OUT std_logic;
        d :IN  std_logic;
        rst:IN  std_logic;
        ce: IN  std_logic;
        clk:IN std_logic
    );
```

```

end gowin_dffre;
ARCHITECTURE rtl OF gowin_dffre IS
begin
    process(clk,rst,ce)
    begin
        if(clk 'event and clk ='1') then
            if(rst='1')then
                q<='0';
            elsif(ce='1')then
                q<=D;
            end if;
        end if;
    end process;
end;

```

3.3.5 Register with Clock Enable and Asynchronous Preset (Verilog)

```

// 1-bit rising-edge clock register
// Active-high asynchronous preset
// Active-high clock enable
module gowin_dffpe(clk, d, ce, preset, q );
input clk, d, ce, preset;
output reg q= 1'b1;
always @(posedge clk or posedge preset )begin
    if (preset)begin
        q <= 1'b1;
    end
    else begin
        if (ce)begin
            q <= d;
        end
    end
end
endmodule

```

3.3.6 Register with Clock Enable and Asynchronous Preset (VHDL)

```

-- 1-bit rising-edge clock register

```

```

-- Active-high asynchronous preset
-- Active-high clock enable
library ieee;
use ieee.std_logic_1164.all;
entity gowin_dffpe IS
PORT(
    q:OUT std_logic;
    d: IN  std_logic;
    clk:IN std_logic;
    ce: IN std_logic;
    preset:IN std_logic
);
end entity;
ARCHITECTURE rtl OF gowin_dffpe IS
begin
    process(clk,preset,ce)
    begin
        if(preset='1')then
            q<='1';
        elsif(clk 'event and clk ='1') then
            if(ce='1') then
                q<=D;
            end if;
        end if;
    end process;
end;
```

3.3.7 Register with Clock Enable and Asynchronous Clear (Verilog)

```

// 1-bit rising-edge clock register
// Active-high asynchronous clear
// Active-high clock enable
module gowin_dffce (clk, d, ce, clear, q );
input clk, d, ce, clear;
output reg q= 1'b0;
always @(posedge clk or posedge clear )begin
```

```

        if (clear)begin
            q <= 1'b0;
        end
        else begin
            if (ce)begin
                q <= d;
            end
        end
    end
end
endmodule

```

3.3.8 Register with Clock Enable and Asynchronous Clear (VHDL)

```

-- 1-bit rising-edge clock register
-- Active-high asynchronous clear
-- Active-high clock enable
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity gowin_dffce IS
    PORT(q:OUT std_logic;
          d : std_logic;
          clk:IN std_logic;
          ce: IN std_logic;
          clear:IN std_logic
    );
end gowin_dffce;
ARCHITECTURE rtl OF gowin_dffce IS
begin
    process(clk,clear,ce)
    begin
        if(clear='1')then
            q<='0';
        elsif(clk 'event and clk ='1') then
            if(ce='1') then
                q<=d;
            end if;
        end if;
    end process;
end rtl;

```



```
        end if;  
    end process;  
end;
```

4 Latches

4.1 Latches

Latches are generally caused by the following situations:

1. Incomplete case statements in combinational logic.
2. Incomplete if-else statements in combinational logic.
3. Continuous assignments or loops in combinational logic.

4.2 Latch Examples

4.2.1 Data Latch with Asynchronous Clear and Latch Enable (Verilog)

```
// Latch with Positive Gate, Asynchronous Clear, and Latch Enable
```

```
// Incomplete case statement conditions lead to latch
```

```
module gowin_dlce(dout,rst,ce,a, b,c,d,select);
```

```
output dout;
```

```
input a,b,c,d;
```

```
input ce,rst;
```

```
input [3:0] select;
```

```
reg dout;
```

```
always @(*)begin
```

```
    if(rst)begin
```

```
        dout<=0;
```

```
    end
```

```
    else begin
```

```
        if(ce)begin
```

```
            case(select)
```

```
                4'b0001: dout<=a;
```

```
                4'b1110: dout<=b;
```

```

        4'b1100: dout<=c;
        4'b1000: dout<=d;
    endcase
end
end
end
endmodule

```

4.2.2 Data Latch with Asynchronous Preset and Latch Enable (Verilog)

```

// Latch with Positive Gate, Asynchronous Preset, and Latch Enable
// Incomplete combinational logic if-else statements lead to latch
module rtl_dlpe (q,d,g, ce,preset);
input d,g, ce,preset;
output reg q= 1'b1;
always @(d or g or preset or ce) begin
    if(preset)begin
        q <= 1'b1;
    end
    else begin
        if (g && ce)begin
            q <= d;
        end
    end
end
end
endmodule

```

4.2.3 Data Latch with Asynchronous Preset and Latch Enable (VHDL)

```

-- Latch with Positive Gate, Asynchronous Preset, and Latch Enable
-- Incomplete combinational logic if-else statements lead to latch
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY rtl_dlpe IS
PORT(d:IN STD_LOGIC;
     g:IN STD_LOGIC;
     preset:IN STD_LOGIC;
     q:OUT STD_LOGIC;

```

```
        ce:IN STD_LOGIC
    );
END rtl_dlpe;
ARCHITECTURE BEH OF rtl_dlpe IS
BEGIN
    PROCESS(g,d,preset,ce)
    BEGIN
        IF (preset='1')THEN
            q <= '1';
        ELSIF(g='1'AND ce='1')THEN
            q<=d;
        END IF;
    END PROCESS;
END;
```

5 Tristate Buffers

5.1 Tristate Buffers

Gowin Synthesis can recognize the following coding styles for tristate buffers:

1. Modeling using concurrent assignments
2. Modeling using if-else structures

5.2 Tristate Buffer Examples

5.2.1 TriState Using Concurrent Assignment (Verilog)

```
// Tristate Description Using Concurrent Assignment
module gowin_tbuf (i, oen, o);
input i,oen;
output o;
assign o= ~oen ? i :1'bz;
endmodule
```

5.2.2 TriState Using Concurrent Assignment (VHDL)

```
-- Tristate Description Using Concurrent Assignment
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity gowin_tbuf is
    PORT (
        o  : out std_logic;
        i  : in   std_logic;
        oen : in   std_logic
    );
end gowin_tbuf;
```

```

architecture Behavioral of gowin_tbuf is
begin
    o <= i when oen = '0' else 'Z';
end Behavioral;

```

5.2.3 Tristate Using Combinatorial Logic (Verilog)

```

// Tristate Description Using Combinatorial Always Block
module gowin_tbuf (i, oen, o);
input i, oen;
output reg o;
reg data_out;
always@(oen,i)begin
    if(~oen)
        o <=i;
    else
        o <=1'bz;
end
endmodule

```

5.2.4 Tristate Using Combinatorial Logic (VHDL)

```

-- Tristate Description Using Combinatorial Process
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity gowin_tbuf is
    PORT (
        o : OUT    std_logic;
        i : IN     std_logic;
        oen : IN    std_logic
    );
end gowin_tbuf;
architecture Behavioral of gowin_tbuf is
begin
    process( i, oen) begin
        if ((oen = '0') or (oen = 'L')) then
            o <= i;
        elsif ((oen = '1') or (oen = 'H')) then

```

```
        o <= 'Z';  
    else  
        o <= 'X';  
    end if;  
    end process;  
end Behavioral;
```

6 Bidirectional Buffers

6.1 Bidirectional Buffers

Gowin Synthesis can recognize the following coding styles for bidirectional buffers:

1. Modeling using concurrent assignments
2. Modeling using if-else structures

6.2 Bidirectional Buffer Examples

6.2.1 Bidirectional Using Concurrent Assignment (Verilog)

```
// Bidirectional Description Using Concurrent Assignment
module gowin_iobuf (i, oen, io, o);
input i, oen;
output o;
inout io;
assign io= ~oen ? i :1'bz;
assign o = io;
endmodule
```

6.2.2 Bidirectional Using Concurrent Assignment (VHDL)

```
-- Bidirectional Description Using Concurrent Assignment
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity gowin_iobuf is
    PORT (
        o : OUT std_logic;
        io : INOUT std_logic;
```



```

        i : IN    std_logic;
        oen : IN   std_logic
    );
end entity;
architecture Behavioral of gowin_iobuf is
begin
    o<=io;
    io <= i when oen = '0' else  'Z';
end Behavioral;

```

6.2.3 Bidirectional Using Combinatorial Logic (Verilog)

```

// Bidirectional Description Using Combinatorial Always Block
module gowin_iobuf (i, oen,  io, o);
input i,oen;
output  o;
inout io;
reg data_out;
always@(oen,i)begin
    if(~oen)
        data_out<=i;
    else
        data_out<=1'bz;
end
assign io= data_out;
assign o = io;
endmodule

```

6.2.4 Bidirectional Using Combinatorial Logic (VHDL)

```

-- Bidirectional Description Using Combinatorial Process
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity gowin_iobuf is
    PORT (
        o : OUT    std_logic;
        io : INOUT std_logic;

```

```
        i : IN      std_logic;
        oen : IN     std_logic
    );
end entity;

architecture Behavioral of gowin_jobuf is
begin
    process(io, i, oen)
    begin
        o <= TO_X01(io);
        if ((oen = '0') or (oen = 'L')) then
            io <= i;
        elsif ((oen = '1') or (oen = 'H')) then
            io <= 'Z';
        else
            io <= 'X';
        end if;
    end process;

end Behavioral;
```

7 Shift Registers

7.1 Static Shift Registers

A static shift register consists of a series of flip-flops that allow data to be transferred through a fixed number of delay stages.

7.1.1 Static Shift Registers

Static shift registers typically include the following elements:

- Clock
- Optional clock enable
- Serial data input
- Serial data output

7.1.2 Static Shift Register Examples

32-Bit Shift Register Using Concatenation (Verilog)

```
// 32-bit Shift Register
// Rising edge clock
// Active high clock enable
module gowin_ram16sdp1 (clk,ce,din,dout);
parameter depth=32;
input clk;
input ce;
input din;
output dout;

reg [depth-1:0]shreg;

always@(posedge clk)begin
    if(ce)begin
```

```

        shreg<={shreg[depth-2:0],din};
    end
end
assign dout=shreg[depth-1];
endmodule

```

32-Bit Shift Register Using Concatenation (VHDL)

```

-- 32-bit Shift Register
-- Rising edge clock
-- Active high clock enable
library ieee;
use ieee.std_logic_1164.all;
entity gowin_ram16sdp1 is
    generic(
        DEPTH : integer := 32
    );
    port(
        clk : in std_logic;
        din : in std_logic;
        ce : in std_logic;
        dout : out std_logic
    );
end gowin_ram16sdp1;

architecture rtl of gowin_ram16sdp1 is
    signal shreg : std_logic_vector(DEPTH - 1 downto 0);
begin
    process(clk)
    begin
        if rising_edge(clk) then
            if ce = '1' then
                shreg <= shreg(DEPTH - 2 downto 0) & din;
            end if;
        end if;
    end process;
    dout <= shreg(DEPTH - 1);
end

```

```
end rtl;
```

32-Bit Shift Register Using For Loop (Verilog)

```
// 32-bit shift register
// Rising-edge clock
// Active-high clock enable
module gowin_ram16sdp1(clk, ce, din, dout);
parameter depth=32;
input clk, ce;
input  din;
output  dout;
reg [depth-1:0]regBank;
integer i;
always @(posedge clk) begin
    if (ce) begin
        for (i = 0; i < depth-1; i = i+1)
            regBank[i+1] <= regBank[i];
        regBank[0] <= din;
    end
end
assign dout = regBank[depth-1];
endmodule
```

32-Bit Shift Register Using For Loop (VHDL)

```
-- 32-bit shift register
-- Rising-edge clock
-- Active-high clock enable
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity gowin_ram16sdp1 is
    generic(
        depth: integer := 32
    );
    port(
        clk : in std_logic;
        ce  : in std_logic;
```

```

        din : in std_logic;
        dout : out std_logic

    );
end entity;
architecture Behavioral of gowin_ram16sdp1 is
    signal regBank: std_logic_vector(depth-1 downto 0);
begin
    PROCESS(clk) begin
        IF(clk'event and clk = '1') then
            IF (ce = '1') then
                for i in 1 to depth-1 loop
                    regBank(i) <= regBank(i-1);
                end loop;
                regBank(0) <= din;
            end IF;
        end IF;
    end PROCESS;
    dout <= regBank(depth-1);
END Behavioral;

```

7.2 Dynamic Shift Registers

A dynamic shift register is a type of shift register whose length can be dynamically changed during circuit operation.

7.2.1 Dynamic Shift Registers

Dynamic shift registers typically include the following elements:

- Clock
- Optional clock enable
- Serial data input
- Serial address input
- Serial data output

7.2.2 Dynamic Shift Register Examples

32-Bit Dynamic Shift Register Using Concatenation (Verilog)

```

// 32-bit dynamic shift register.
module gowin_dffe(clk, ce, din,addr, dout);
    parameter width_addr=5;

```

```

parameter depth=2**width_addr;
input clk, ce;
input  din;
input [width_addr-1:0] addr;
output reg dout;
reg dout_reg;
reg [depth-1:0] regBank;
always @(posedge clk) begin
    if (ce) begin
        regBank <= {regBank[depth-2:0],din};
    end
end
always @(posedge clk) begin
    if (ce) begin
        dout <= dout_reg;
        dout_reg<=regBank[addr];
    end
end
endmodule

```

32-Bit Dynamic Shift Register Using Concatenation (VHDL)

```

--32-bit dynamic shift register
Library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity gowin_dffre is
    generic(
        width_addr: integer := 5;
        depth: integer := 2**width_addr
    );
    port(
        clk : in std_logic;
        ce : in std_logic;
        din : in std_logic;
        addr : in std_logic_vector(width_addr-1 downto 0);
        dout : out std_logic
    );
end entity

```

```

    );
end entity;

architecture Behavioral of gowin_dffre is
    signal regBank: std_logic_vector(depth-1 downto 0);
    signal dout_reg : std_logic;
begin
    PROCESS(clk) begin
        IF(clk'event and clk = '1') then
            IF (ce = '1') then
                regBank <= regBank(depth-2 downto 0) & din;
            end IF;
        end IF;
    end PROCESS;
    PROCESS(clk) begin
        IF(clk'event and clk = '1') then
            IF (ce = '1') then
                dout <= dout_reg;
                dout_reg<=regBank(conv_integer(addr));
            end if;
        end IF;
    end PROCESS;
END Behavioral;

```

32-Bit Dynamic Shift Register Using For Loop (Verilog)

```

// 32-bit dynamic shift register
module gowin_dffe(clk, ce,addr, din, dout);
parameter addr_width=5;
parameter depth=2**addr_width;
input clk, ce;
input din;
input[addr_width-1:0]addr;
output reg dout;
reg dout_reg;
reg [depth-1:0]regBank;
integer i;

```



```

always @(posedge clk) begin
    if (ce) begin
        for (i = 0; i < depth-1; i = i+1)
            regBank[i+1] <= regBank[i];
        regBank[0] <= din;
    end
end
always @(posedge clk) begin
    if (ce) begin
        dout <= dout_reg;
        dout_reg <= regBank[addr];
    end
end
endmodule

```

32-Bit Dynamic Shift Register Using For Loop (VHDL)

```

-- 32-bit dynamic shift register
Library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity gowin_dffre is
    generic(
        width_addr: integer := 5;
        depth: integer := 2**width_addr
    );
    port(
        clk : in std_logic;
        ce : in std_logic;
        din : in std_logic;
        addr : in std_logic_vector(width_addr-1 downto 0);
        dout : out std_logic
    );
end entity;
architecture Behavioral of gowin_dffre is
    signal regBank: std_logic_vector(depth-1 downto 0);
    signal dout_reg : std_logic;

```

```
begin
  PROCESS(clk) begin
    IF(clk'event and clk = '1') then
      IF (ce = '1') then
        for i in 1 to depth-1 loop
          regBank(i) <= regBank(i-1);
        end loop;
        regBank(0) <= din;
      end IF;
    end IF;
  end PROCESS;
  PROCESS(clk) begin
    IF(clk'event and clk = '1') then
      IF (ce = '1') then
        dout <= dout_reg;
        dout_reg<=regBank(conv_integer(addr));
      end if;
    end IF;
  end PROCESS;
END Behavioral;
```

8RAM

Gowin Synthesis supports various RAM coding styles and maps them to either Shadow Static Random Access Memory (SSRAM) or Block Static Random Access Memory (BSRAM).

RAM coding typically includes the following elements:

- Support for arbitrary sizes and data widths. Gowin Synthesis maps the RAM to one or more RAM primitives, such as Single-Port, Semi Dual-Port, and Dual-Port.
- Up to two write ports.
- Up to two read ports.
- RAM write enable (BSRAM).
- Data output reset (BSRAM).
- Optional output registers (BSRAM).
- Byte write enable (BSRAM).
- Each RAM port can be controlled by its own clock, port enable, write enable, and data output reset signals.
- RAM initialization.

Note!

Read and write operations must not be performed simultaneously on the same RAM address.

8.1 BSRAM

8.1.1 Single-Port BSRAM Examples

Single-Port BSRAM with Read-After-Write Mode (Verilog)

```
// Single-Port Block RAM Write-First Mode
module gowin_spx9(data_out, data_in, addr, clk, oce, ce, wre, rst);
    output reg [17:0] data_out;
    input [17:0] data_in;
    input [9:0] addr;
```

```
input clk,wre,oce,ce,rst;
reg [17:0] mem [1023:0];
reg [17:0]data_out_reg;

always@(posedge clk )begin
    if(rst)begin
        data_out <= 0;
    end
    else begin
        if(oce)begin
            data_out <= data_out_reg;
        end
    end
end

always@(posedge clk )begin
    if(rst)begin
        data_out_reg <= 0;
    end
    else begin
        if(ce & wre)begin
            data_out_reg <= data_in;
        end
        else begin
            if (ce & !wre)begin
                data_out_reg <= mem[addr];
            end
        end
    end
end

always @(posedge clk)begin
    if (ce & wre)begin
        mem[addr] <= data_in;
    end
end
```

```
endmodule
```

Single-Port BSRAM with Read-After-Write Mode (VHDL)

```
-- Single-Port Block RAM Write-First Mode
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
use IEEE.std_logic_unsigned.all;
```

```
entity gowin_spx9 is
```

```
    generic(
```

```
        DATA_WIDTH : integer := 18;
```

```
        ADDRESS_WIDTH : integer := 10
```

```
    );
```

```
    port (
```

```
        data_in : in STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0);
```

```
        addr: in STD_LOGIC_VECTOR(ADDRESS_WIDTH - 1 downto 0);
```

```
        clk, oce, ce, wre,rst: in STD_LOGIC;
```

```
        data_out : out STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0)
```

```
    );
```

```
end gowin_spx9;
```

```
architecture rtl of gowin_spx9 is
```

```
    type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
        STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);
```

```
    signal mem : mem_type;
```

```
    signal data_out_reg : STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0);
```

```
begin
```

```
    process (clk)
```

```
    begin
```

```
        if (rising_edge(clk)) then
```

```
            if(ce = '1'and wre='1')then
```

```
                mem(conv_integer(addr)) <= data_in;
```

```
            end if;
```

```
        end if;
```

```

end process;

process (clk)
begin
    if (rising_edge(clk)) then
        if(rst = '1')then
            data_out_reg<=(others=>'0');
        else
            if(ce = '1')then
                if(wre='1')then
                    data_out_reg <= data_in;
                else
                    data_out_reg <=
mem(conv_integer(addr));
                end if;
            end if;
        end if;
    end if;
end process;

```

```

process (clk)
begin
    if (rising_edge(clk)) then
        if(rst = '1')then
            data_out<=(others=>'0');
        else
            if(oce = '1')then
                data_out <= data_out_reg;
            end if;
        end if;
    end if;
end process;

end rtl;

```

Single-Port BSRAM with Read-Before-Write Mode (Verilog)

// Single-Port Block RAM Read-First Mode

```
module gowin_spx9(data_out, data_in, addr, clk, oce, ce, wre, rst);
output reg [17:0]data_out;
input [17:0]data_in;
input [9:0]addr;
input clk, wre, oce, ce, rst;
reg [17:0] mem [1023:0];
reg [17:0]data_out_reg;

always@(posedge clk )begin
    if(rst)begin
        data_out <= 0;
    end
    else begin
        if(oce)begin
            data_out <= data_out_reg;
        end
    end
end

always@(posedge clk )begin
    if(rst)begin
        data_out_reg <= 0;
    end
    else begin
        if(ce )begin
            data_out_reg <= mem[addr];
        end
    end
end

always @(posedge clk)begin
    if (ce & wre)begin
        mem[addr] <= data_in;
    end
end
endmodule
```

Single-Port BSRAM with Read-Before-Write Mode (VHDL)

```

-- Single-Port Block RAM Read-First Mode
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity gowin_spx9 is
    generic(
        DATA_WIDTH : integer := 18;
        ADDRESS_WIDTH : integer := 10
    );
    port (
        data_in : in STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto
0);
        addr: in STD_LOGIC_VECTOR(ADDRESS_WIDTH - 1
downto 0);
        clk, oce, ce, wre,rst: in STD_LOGIC;
        data_out : out STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0)
    );
end gowin_spx9;

architecture rtl of gowin_spx9 is
    type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
        STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);
    signal mem : mem_type;
    signal data_out_reg : STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0);
begin
    process (clk)
    begin
        if (rising_edge(clk)) then
            if(ce = '1'and wre='1')then
                mem(conv_integer(addr)) <= data_in;
            end if;
        end if;
    end process;
end rtl;

```



```

process (clk)
begin
    if (rising_edge(clk)) then
        if(rst = '1')then
            data_out_reg<=(others=>'0');
        else
            if(ce = '1')then
                data_out_reg <= mem(conv_integer(addr));
            end if;
        end if;
    end if;
end process;

process (clk)
begin
    if (rising_edge(clk)) then
        if(rst = '1')then
            data_out<=(others=>'0');
        else
            if(oce = '1')then
                data_out <= data_out_reg;
            end if;
        end if;
    end if;
end process;
end rtl;

```

Single-Port BSRAM in Normal Mode (Verilog)

```

// Single-Port Block RAM Normal Mode
module gowin_spx9(data_out, data_in, addr, clk,oce,ce, wre,rst);
output reg [17:0]data_out;
input [17:0]data_in;
input [9:0]addr;
input clk,wre,oce,ce,rst;
reg [17:0] mem [1023:0];

```

```

reg [17:0]data_out_reg;

always@(posedge clk )begin
    if(rst)begin
        data_out <= 0;
    end
    else begin
        if(oce)begin
            data_out <= data_out_reg;
        end
    end
end

always@(posedge clk )begin
    if(rst)begin
        data_out_reg <= 0;
    end
    else begin
        if(ce & !wre)begin
            data_out_reg <= mem[addr];
        end
    end
end

always @(posedge clk)begin
    if (ce & wre)begin
        mem[addr] <= data_in;
    end
end
endmodule

```

Single-Port BSRAM in Normal Mode (VHDL)

```

-- Single-Port Block RAM Normal Mode
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity gowin_spx9 is

```

```

generic(
    DATA_WIDTH : integer := 18;
    ADDRESS_WIDTH : integer := 10
);
port (
    data_in : in STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto
0);
    addr: in STD_LOGIC_VECTOR(ADDRESS_WIDTH - 1
downto 0);
    clk, oce, ce, wre,rst: in STD_LOGIC;
    data_out : out STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0)
);
end gowin_spx9;

```

architecture rtl of gowin_spx9 is

```

    type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);
    signal mem : mem_type;
    signal data_out_reg : STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0);
begin
    process (clk)
    begin
        if (rising_edge(clk)) then
            if(ce = '1'and wre='1')then
                mem(conv_integer(addr)) <= data_in;
            end if;
        end if;
    end process;

    process (clk)
    begin
        if (rising_edge(clk)) then
            if(rst = '1')then
                data_out_reg<=(others=>'0');

```

```

        else
            if(ce = '1' and wre = '0')then
                data_out_reg <= mem(conv_integer(addr));
            end if;
        end if;
    end if;
end process;

process (clk)
begin
    if (rising_edge(clk)) then
        if(rst = '1')then
            data_out<=(others=>'0');
        else
            if(oce = '1')then
                data_out <= data_out_reg;
            end if;
        end if;
    end if;
end process;
end rtl;

```

8.1.2 Semi Dual-Port BSRAM Examples

Semi Dual-Port BSRAM with One Clock (Verilog)

```

// Semi Dual-Port Block RAM with One Clock
module gowin_sdpb(dout, din, ada, adb, clk,oce, cea, ceb, resetb);
    output reg[15:0]dout;
    input [15:0]din;
    input [9:0]ada, adb;
    input clk,oce, cea, ceb, resetb;
    reg [15:0] mem [1023:0];
    reg[15:0]dout_reg;
    always @(posedge clk)begin
        if (cea )begin
            mem[ada] <= din;

```

```

        end
    end

    always@(posedge clk)begin
        if(resetb)begin
            dout <= 0;
        end
        else if(oce)begin
            dout <= dout_reg;
        end
    end
end

always@(posedge clk)begin
    if(resetb)begin
        dout_reg <= 0;
    end
    else if(ceb)begin
        dout_reg <= mem[adb];
    end
end
endmodule

```

Semi Dual-Port BSRAM with One Clock (VHDL)

-- Semi Dual-Port Block RAM with One Clock

library IEEE;

use IEEE.std_logic_1164.all;

use IEEE.std_logic_unsigned.all;

entity gowin_sdpb is

generic(

 DATA_WIDTH : integer := 16;

 ADDRESS_WIDTH : integer := 10

);

port (

 din : in STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0);

 ada, adb: in STD_LOGIC_VECTOR(ADDRESS_WIDTH - 1

```

downto 0);
        clk,oce, cea, ceb,resetb: in STD_LOGIC;
        dout : out STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto
0));
    end gowin_sdpb;

```

architecture rtl of gowin_sdpb is

```

    type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);
    signal mem : mem_type;
    signal dout_reg : STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0);

```

begin

```

    process(clk)
    begin
        if (rising_edge(clk)) then
            if (resetb='1')then
                dout <=(others=>'0');
            else
                if(oce = '1')then
                    dout <= dout_reg;
                end if;
            end if;
        end if;
    end process;

```

```

    process(clk)
    begin
        if (rising_edge(clk)) then
            if (resetb='1')then
                dout_reg <=(others=>'0');
            else
                if(ceb = '1')then
                    dout_reg <= mem(conv_integer(adb));
                end if;
            end if;
        end if;
    end process;

```

```

        end if;
    end if;
end process;

process (clk)
begin
    if (rising_edge(clk)) then
        if(cea = '1')then
            mem(conv_integer(ada)) <= din;
        end if;
    end if;
end process;
end rtl;

```

Semi Dual-Port BSRAM with Two Clocks (Verilog)

```

// Semi Dual-Port Block RAM with two Clock
module gowin_sdpb(dout, din, ada, adb, clka, oce, cea, clkb, ceb,
resetb);
    output reg[15:0]dout;
    input [15:0]din;
    input [9:0]ada, adb;
    input clka, oce, cea, clkb, ceb, resetb;
    reg [15:0] mem [1023:0];
    reg[15:0]dout_reg;
    always @(posedge clka)begin
        if (cea )begin
            mem[ada] <= din;
        end
    end

    always@(posedge clkb)begin
        if(resetb)begin
            dout <= 0;
        end
        else if(oce)begin
            dout <= dout_reg;
        end
    end
endmodule

```

```

        end
    end

    always@(posedge clkb)begin
        if(resetb)begin
            dout_reg <= 0;
        end
        else if(ceb)begin
            dout_reg <= mem[adb];
        end
    end
end
endmodule

```

Semi Dual-Port BSRAM with Two Clocks (VHDL)

```

-- Semi Dual-Port Block RAM with two Clock
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity gowin_sdpb is
    generic(
        DATA_WIDTH : integer := 16;
        ADDRESS_WIDTH : integer := 10
    );
    port (
        din : in STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0);
        ada, adb: in STD_LOGIC_VECTOR(ADDRESS_WIDTH - 1
downto 0);
        clka,oce, cea, clkb, ceb,resetb: in STD_LOGIC;
        dout : out STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto
0));
    end gowin_sdpb;

    architecture rtl of gowin_sdpb is
        type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
            STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);

```



```

        signal mem : mem_type;
        signal dout_reg : STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0);
    begin
        process(clkb)
        begin
            if (rising_edge(clkb)) then
                if (resetb='1')then
                    dout <=(others=>'0');
                else
                    if(oce = '1')then
                        dout <= dout_reg;
                    end if;
                end if;
            end if;
        end process;

        process(clkb)
        begin
            if (rising_edge(clkb)) then
                if (resetb='1')then
                    dout_reg <=(others=>'0');
                else
                    if(ceb = '1')then
                        dout_reg <= mem(conv_integer(adb));
                    end if;
                end if;
            end if;
        end process;

        process (clka)
        begin
            if (rising_edge(clka)) then
                if(cea = '1')then
                    mem(conv_integer(ada)) <= din;

```

```

        end if;
    end if;
end process;
end rtl;

```

Asymmetric RAM Examples

Asymmetric RAM with Read Wider Than Write (Verilog)

```

// Asymmetric port RAM
// Read Wider than Write
module gowin_sdpb(dout, din, ada, clka, oce, cea, adb, clkb, ceb, rstb);
parameter adawidth = 8;
parameter diwidth = 6;
parameter adbwidth = 7;
parameter dowidth = 12;

output reg[dowidth-1:0]dout;
input [diwidth-1:0]din;
input [adawidth-1:0]ada;
input [adbwidth-1:0]adb;
input clka, cea, clkb, ceb, oce, rstb;
reg [diwidth-1:0]mem [2**adawidth-1:0];
reg [dowidth-1:0]dout_reg;
localparam b = 2**adawidth/2**adbwidth ;
integer j ;

always @(posedge clka)begin
    if (cea)begin
        mem[ada] <= din;
    end
end

always@(posedge clkb )begin
    if(rstb)begin
        dout_reg <= 0;
    end
    else begin

```

```

        if(ceb)begin
            for(j = 0;j < b;j = j+1)
                dout_reg[((j+1)*diwidth-1)-: diwidth]<=
mem[adb*b+j];
            end
        end
    end
    always@(posedge clkb )begin
        if(rstb)begin
            dout <= 0;
        end
        else begin
            if(oce)begin
                dout <= dout_reg;
            end
        end
    end
end
endmodule

```

Asymmetric RAM with Read Wider Than Write (VHDL)

```

-- Asymmetric port RAM
-- Read Wider than Write
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity gowin_sdpb is
    generic(
        DATA_WIDTHB : integer := 12;
        ADDRESS_WIDTHB : integer := 7;
        ADDRESS_WIDTHA : integer := 8;
        DATA_WIDTHA : integer := 6
    );
    port (
        din : in STD_LOGIC_VECTOR(DATA_WIDTHA - 1 downto
0);
        ada: in STD_LOGIC_VECTOR(ADDRESS_WIDTHA - 1
downto 0);

```

```

        clka, cea, clkb, oce, ceb, rstb: in STD_LOGIC;
        adb: in STD_LOGIC_VECTOR(ADDRESS_WIDTHB - 1
downto 0);
        dout : out STD_LOGIC_VECTOR(DATA_WIDTHB - 1 downto
0)
    );
end gowin_sdpb;

```

architecture rtl of gowin_sdpb is

```

    type mem_type is array (2**ADDRESS_WIDTHA - 1 downto 0) of
STD_LOGIC_VECTOR (DATA_WIDTHA - 1 downto 0);
    signal dout_reg : STD_LOGIC_VECTOR(DATA_WIDTHB - 1
downto 0);
    signal mem : mem_type;
begin
    process (clka)
    begin
        if (rising_edge(clka)) then
            if(cea = '1')then
                mem(conv_integer(ada)) <= din;
            end if;
        end if;
    end process;
    process(clkb)
    begin
        if (rising_edge(clkb)) then
            if (rstb='1')then
                dout_reg <=(others=>'0');
            else
                if(ceb = '1')then
                    dout_reg(DATA_WIDTHA*1 - 1 downto
DATA_WIDTHA*0) <= mem(conv_integer(adb&'0'));
                    dout_reg(DATA_WIDTHA*2 - 1 downto
DATA_WIDTHA*1) <= mem(conv_integer(adb&'1'));
                end if;
            end if;
        end if;
    end process;
end rtl;

```

```

        end if;
    end process;
    process(clkb)
    begin
        if (rising_edge(clkb)) then
            if (rstb='1')then
                dout <=(others=>'0');
            else
                if(oce = '1')then
                    dout <= dout_reg;
                end if;
            end if;
        end if;
    end process;
end rtl;

```

Asymmetric RAM with Write Wider Than Read (Verilog)

```

// Asymmetric port RAM
// Write wider than Read
module gowin_sdpb(dout, din, ada, clka, oce, cea, adb, clkb, ceb, rstb);
    parameter adawidth = 10;
    parameter diwidth = 16;
    parameter adbwidth = 11;
    parameter dowidth = 8;

    output reg[dowidth-1:0]dout;
    input [diwidth-1:0]din;
    input [adawidth-1:0]ada;
    input [adbwidth-1:0]adb;
    input clka, cea, clkb, ceb, oce, rstb;
    reg [dowidth-1:0]mem [2**adbwidth-1:0];
    reg [dowidth-1:0]dout_reg;

    always @(posedge clka)begin
        if (cea)begin
            mem[{ada, 1'b0}] <= din[dowidth*0+:dowidth];

```

```

        mem[{ada,1'b1}] <= din[dowidth*1+:dowidth];
    end
end

always@(posedge clkb )begin
    if(rstb)begin
        dout_reg <= 0;
    end
    else begin
        if(ceb)begin
            dout_reg<= mem[adb];
        end
    end
end
end
always@(posedge clkb )begin
    if(rstb)begin
        dout <= 0;
    end
    else begin
        if(oce)begin
            dout <= dout_reg;
        end
    end
end
end
endmodule

```

Asymmetric RAM with Write Wider Than Read (VHDL)

```

-- Asymmetric port RAM
-- Write wider than Read
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity gowin_sdpb is
    generic(
        DATA_WIDTHHB : integer := 8;
        ADDRESS_WIDTHHB : integer := 11;

```

```

        ADDRESS_WIDTHA : integer := 10;
        DATA_WIDTHA : integer := 16
    );
    port (
        din : in STD_LOGIC_VECTOR(DATA_WIDTHA - 1 downto
0);
        ada: in STD_LOGIC_VECTOR(ADDRESS_WIDTHA - 1
downto 0);
        clka, cea, clkb, oce, ceb, rstb: in STD_LOGIC;
        adb: in STD_LOGIC_VECTOR(ADDRESS_WIDTHB - 1
downto 0);
        dout : out STD_LOGIC_VECTOR(DATA_WIDTHB - 1 downto
0)
    );
end gowin_sdpb;

```

architecture rtl of gowin_sdpb is

```

    type mem_type is array (2**ADDRESS_WIDTHB - 1 downto 0) of
STD_LOGIC_VECTOR (DATA_WIDTHB - 1 downto 0);

```

```

    signal dout_reg : STD_LOGIC_VECTOR(DATA_WIDTHB - 1
downto 0);

```

```

    signal mem : mem_type;

```

```

begin

```

```

    process (clka)

```

```

    begin

```

```

        if (rising_edge(clka)) then

```

```

            if(cea = '1')then

```

```

                mem(conv_integer(ada & '0')) <=
din(DATA_WIDTHB*1-1 downto DATA_WIDTHB*0);

```

```

                mem(conv_integer(ada & '1')) <=
din(DATA_WIDTHB*2-1 downto DATA_WIDTHB*1);

```

```

            end if;

```

```

        end if;

```

```

    end process;

```

```

    process(clkb)

```

```

    begin

```

```

        if (rising_edge(clkb)) then

```

```

        if (rstb='1')then
            dout_reg <=(others=>'0');
        else
            if(ceb = '1')then
                dout_reg<= mem(conv_integer(adb));
            end if;
        end if;
    end if;
end process;
process(clkb)
begin
    if (rising_edge(clkb)) then
        if (rstb='1')then
            dout <=(others=>'0');
        else
            if(oce = '1')then
                dout <= dout_reg;
            end if;
        end if;
    end if;
end process;
end rtl;

```

8.1.3 Dual-Port BSRAM Examples

Dual-Port BSRAM with Write-Before-Read Mode (Verilog)

```

// Dual-Port Block RAM Write-First Mode
module gowin_dpb(data_outa, data_ina, addra, clka, cea, ocea, wrea,
rsta, data_outb, data_inb, addrb, clkb, ceb, oceb, wreb, rstb);
    output reg [15:0]data_outa,data_outb;
    input [15:0]data_ina,data_inb;
    input [9:0]addra,addrb;
    input clka,wrea,cea,ocea,rsta;
    input clkb,wreb,ceb,oceb,rstb;
    reg [15:0] mem [1023:0];
    reg [15:0] data_outa_reg=16'h0000;
    reg [15:0] data_outb_reg=16'h0000;

```



```

always@(posedge clka)begin
    if(rsta)begin
        data_outa <= 0;
    end
    else begin
        if (oceas)begin
            data_outa <= data_outa_reg;
        end
    end
end
always@(posedge clka)begin
    if(rsta)begin
        data_outa_reg <= 0;
    end
    else begin
        if(ceas)begin
            if(!wreas)begin
                data_outa_reg <= mem[addra];
            end
            else begin
                data_outa_reg <= data_ina;
            end
        end
    end
end
always @(posedge clka)begin
    if (ceas & wreas) begin
        mem[addra] <= data_ina;
    end
end

always@(posedge clkb )begin
    if(rstb)begin
        data_outb <= 0;
    end

```

```

        else begin
            if (oceb)begin
                data_outb <= data_outb_reg;
            end
        end
    end
end
always@(posedge clkb )begin
    if(rstb)begin
        data_outb_reg <= 0;
    end
    else begin
        if(ceb)begin
            if(!wreb)begin
                data_outb_reg <= mem[addrb];
            end
            else begin
                data_outb_reg <= data_inb;
            end
        end
    end
end
end

always @(posedge clkb)begin
    if (ceb & wreb) begin
        mem[addrb] <= data_inb;
    end
end
endmodule

```

Dual-Port BSRAM with Write-Before-Read Mode (VHDL)

-- Dual-Port Block RAM Write-First Mode

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

```

```

entity gowin_dpb is

```

```

generic(
    DATA_WIDTH : integer := 16;
    ADDRESS_WIDTH : integer := 10
);
port (
    data_ina, data_inb : in STD_LOGIC_VECTOR(DATA_WIDTH
- 1 downto 0);
    addra, addrb: in STD_LOGIC_VECTOR(ADDRESS_WIDTH
- 1 downto 0);
    clka, cea, ocea,wrea,rsta, clk, ceb, oceb,wreb,rstb: in
STD_LOGIC;
    data_outa, data_outb : out
STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0)
);
end gowin_dpb;

```

architecture rtl of gowin_dpb is

```

    type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);
    signal mem : mem_type;
    signal data_outa_reg, data_outb_reg :
STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0);
begin
    process(clka)
    begin
        if (rising_edge(clka)) then
            if(cea = '1' and wrea = '1') then
                mem(conv_integer(addra)) <= data_ina;
            end if;
        end if;
    end process;
    process(clka)
    begin
        if (rising_edge(clka)) then
            if(rsta='1')then
                data_outa_reg<=(others=>'0');
            end if;
        end if;
    end process;

```

```

        else
            if(cea = '1')then
                if(wrea = '0') then
                    data_outa_reg <=
mem(conv_integer(addr_a));
                else
                    data_outa_reg <= data_ina;
                end if;
            end if;
        end if;
    end process;
process(clka)
begin
    if (rising_edge(clka)) then
        if(rsta='1')then
            data_outa<=(others=>'0');
        else
            if(ocea = '1') then
                data_outa <= data_outa_reg;
            end if;
        end if;
    end if;
end process;

process (clkb)
begin
    if (rising_edge(clkb)) then
        if(rstb='1')then
            data_outb <= (others=>'0');
        else
            if(oceb = '1') then
                data_outb <= data_outb_reg;
            end if;
        end if;
    end if;
end process;

```

```

        end if;
    end process;
    process (clkb)
    begin
        if (rising_edge(clkb)) then
            if(rstb='1')then
                data_outb_reg <= (others=>'0');
            else
                if(ceb = '1')then
                    if(wreb = '0') then
                        data_outb_reg <=
mem(conv_integer(addrb));
                    else
                        data_outb_reg <= data_inb;
                    end if;
                end if;
            end if;
        end if;
    end process;
    process(clkb)
    begin
        if (rising_edge(clkb)) then
            if(ceb = '1' and wreb = '1') then
                mem(conv_integer(addrb)) <= data_inb;
            end if;
        end if;
    end process;
end rtl;

```

Dual-Port BSRAM in Normal Mode (Verilog)

```

// Dual-Port Block RAM Normal Mode
module gowin_dpb(data_outa, data_ina, addra, clka, cea, ocea, wrea,
rsta, data_outb, data_inb, addrb, clkb, ceb, oceb, wreb, rstb);
    output reg [15:0]data_outa,data_outb;
    input [15:0]data_ina,data_inb;
    input [9:0]addra,addrb;

```

```
input clka,wrea,cea,ocea,rsta;
input clkb,wreb,ceb,oceb,rstb;
reg [15:0] mem [1023:0];
reg [15:0] data_outa_reg=16'h0000;
reg [15:0] data_outb_reg=16'h0000;
always@(posedge clka)begin
    if(rsta)begin
        data_outa <= 0;
    end
    else begin
        if (ocea)begin
            data_outa <= data_outa_reg;
        end
    end
end
always@(posedge clka)begin
    if(rsta)begin
        data_outa_reg <= 0;
    end
    else begin
        if(cea & !wrea)begin
            data_outa_reg <= mem[addra];
        end
    end
end
always @(posedge clka)begin
    if (cea & wrea) begin
        mem[addra] <= data_ina;
    end
end

always@(posedge clkb )begin
    if(rstb)begin
        data_outb <= 0;
    end
end
```

```

        else begin
            if (oceb)begin
                data_outb <= data_outb_reg;
            end
        end
    end
end
always@(posedge clkb )begin
    if(rstb)begin
        data_outb_reg <= 0;
    end
    else begin
        if(ceb & !wreb)begin
            data_outb_reg <= mem[addrb];
        end
    end
end
end

always @(posedge clkb)begin
    if (ceb & wreb) begin
        mem[addrb] <= data_inb;
    end
end
endmodule

```

Dual-Port BSRAM in Normal Mode (VHDL)

```

-- Dual-Port Block RAM Normal Mode
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity gowin_dpb is
    generic(
        DATA_WIDTH : integer := 16;
        ADDRESS_WIDTH : integer := 10
    );
    port (

```

```

        data_ina, data_inb : in STD_LOGIC_VECTOR(DATA_WIDTH
- 1 downto 0);
        addra, addrb: in STD_LOGIC_VECTOR(ADDRESS_WIDTH
- 1 downto 0);
        clka, cea, ocea,wrea,rsta, clk b, ceb, oceb,wreb,rstb: in
STD_LOGIC;
        data_outa, data_outb : out
STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0)
    );
end gowin_dpb;

```

architecture rtl of gowin_dpb is

```

    type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);
    signal mem : mem_type;
    signal data_outa_reg, data_outb_reg :
STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0);
begin
    process(clka)
    begin
        if (rising_edge(clka)) then
            if(cea = '1' and wrea = '1') then
                mem(conv_integer(addra)) <= data_ina;
            end if;
        end if;
    end process;
    process(clka)
    begin
        if (rising_edge(clka)) then
            if(rsta='1')then
                data_outa_reg<=(others=>'0');
            else
                if(cea = '1' and wrea = '0') then
                    data_outa_reg <= mem(conv_integer(addra));
                end if;
            end if;
        end if;
    end process;
end rtl;

```



```

        end if;
    end process;
    process(clka)
    begin
        if (rising_edge(clka)) then
            if(rsta='1')then
                data_outa<=(others=>'0');
            else
                if(ocea = '1') then
                    data_outa <= data_outa_reg;
                end if;
            end if;
        end if;
    end process;

    process (clkb)
    begin
        if (rising_edge(clkb)) then
            if(rstb='1')then
                data_outb <= (others=>'0');
            else
                if(oceb = '1') then
                    data_outb <= data_outb_reg;
                end if;
            end if;
        end if;
    end process;

    process (clkb)
    begin
        if (rising_edge(clkb)) then
            if(rstb='1')then
                data_outb_reg <= (others=>'0');
            else
                if(ceb = '1' and wreb = '0') then
                    data_outb_reg <= mem(conv_integer(addrb));
                end if;
            end if;
        end if;
    end process;

```

```

        end if;
    end if;
end if;
end process;
process(clkb)
begin
    if (rising_edge(clkb)) then
        if(ceb = '1' and wreb = '1') then
            mem(conv_integer(addrb)) <= data_inb;
        end if;
    end if;
end process;
end rtl;

```

8.1.4 Byte-enable

Single-Port BSRAM with Read-Before-Write Mode and and Byte-enable (Verilog)

```

// Single-port BSRAM with Byte-wide Write Enable
// Read-First mode
module gowin_sp (dout, clk, oce, ce, reset, wre, ad, din, byte_en);
output reg[35:0] dout;
input clk,oce,ce,reset,wre;
input [7:0] ad;
input [35:0] din;
input [3:0] byte_en;

reg[35:0]mem[2**8-1:0];
reg[35:0] dout_reg;
always@(posedge clk)begin
    if(ce & wre)begin
        if(byte_en[0])begin
            mem[ad][8:0]<=din[8:0];
        end
        if(byte_en[1])begin
            mem[ad][17:9]<=din[17:9];
        end
    end
end

```

```

        if(byte_en[2])begin
            mem[ad][26:18]<=din[26:18];
        end
        if(byte_en[3])begin
            mem[ad][35:27]<=din[35:27];
        end
    end
end

```

```

always@(posedge clk)begin
    if(reset)begin
        dout_reg<=0;
    end
    else begin
        if(ce)begin
            dout_reg<=mem[ad];
        end
    end
end

```

```

always@(posedge clk)begin
    if(reset)begin
        dout<=0;
    end
    else begin
        if(oce)begin
            dout<=dout_reg;
        end
    end
end
endmodule

```

Single-Port BSRAM with Read-Before-Write Mode and Byte-enable (VHDL)

```

-- Single-port BSRAM with Byte-wide Write Enable
-- Read-First mode

```

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity gowin_sp is
  generic(
    DATA_WIDTH : integer := 36;
    ADDRESS_WIDTH : integer := 8
  );
  port (
    din : in STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0);
    ad: in STD_LOGIC_VECTOR(ADDRESS_WIDTH - 1 downto
0);

    clk,oce,ce, wre,reset: in STD_LOGIC;
    byte_en : in STD_LOGIC_VECTOR(3 downto 0);
    dout : out STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto
0)
  );
end gowin_sp;

architecture rtl of gowin_sp is
  type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
    STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);
  signal mem : mem_type ;
  signal dout_reg : STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0);
begin
  process (clk)
  begin
    if (rising_edge(clk)) then
      if(reset='1')then
        dout <=(others=>'0');
      else
        if(oce ='1')then
          dout <= dout_reg;
        end if;
      end if;
    end if;
  end process;
end architecture rtl;

```

```

        end if;
    end if;
end process;

process (clk)
begin
    if (rising_edge(clk)) then
        if(reset='1')then
            dout_reg <=(others=>'0');
        else
            if(ce ='1')then
                dout_reg <= mem(conv_integer(ad));
            end if;
        end if;
    end if;
end process;

process (clk)
begin
    if (rising_edge(clk)) then
        if(ce ='1'and wre = '1')then
            if(byte_en(0)='1')then
                mem(conv_integer(ad))(8 downto 0) <= din(8
downto 0);

            end if;
            if(byte_en(1)='1')then
                mem(conv_integer(ad))(17 downto 9) <= din(17
downto 9);

            end if;
            if(byte_en(2)='1')then
                mem(conv_integer(ad))(26 downto 18) <=
din(26 downto 18);

            end if;
            if(byte_en(3)='1')then
                mem(conv_integer(ad))(35 downto 27) <=
din(35 downto 27);

```

```

        end if;
    end if;
    end if;
end process;
end rtl;

```

Dual-Port BSRAM with Write-Before-Read Mode and Byte-enable (Verilog)

```

// Dual-Port BRAM with Byte-wide Write Enable
// Write First mode
module gowin_dpb (douta, doutb, clka, ocea, cea, reseta, wrea,
clk b, oceb, ceb, resetb, wreb, ada, dina, adb, dinb, byte_ena, byte_enb);
    output reg [15:0] douta;
    output reg [15:0] doutb;
    input clka, ocea, cea, reseta, wrea;
    input clk b, oceb, ceb, resetb, wreb;
    input [9:0] ada, adb;
    input [15:0] dina, dinb;
    input [1:0] byte_ena, byte_enb;

    reg[15:0] mem[2**10-1:0];
    reg [15:0] douta_reg, doutb_reg;

    always@(posedge clka)begin
        if(cea & wrea)begin
            if(byte_ena[0])begin
                mem[ada][7:0]<=dina[7:0];
            end
            if(byte_ena[1])begin
                mem[ada][15:8]<=dina[15:8];
            end
        end
    end

    always@(posedge clka)begin
        if(reseta)begin

```

```
        douta_reg<=0;
    end
    else begin
        if(cea)begin
            if(!wrea)begin
                douta_reg<=mem[ada];
            end
            else begin
                if(byte_ena[0])begin
                    douta_reg[7:0]<=dina[7:0];
                end
                else begin
                    douta_reg[7:0]<=mem[ada][7:0];
                end
                if(byte_ena[1])begin
                    douta_reg[15:8]<=dina[15:8];
                end
                else begin
                    douta_reg[15:8]<=mem[ada][15:8];
                end
            end
        end
    end
end

always@(posedge clka)begin
    if(reseta)begin
        douta<=0;
    end
    else begin
        if(ocea)begin
            douta<=douta_reg;
        end
    end
end
end
```

```
always@(posedge clkb)begin
    if(ceb & wreb)begin
        if(byte_enb[0])begin
            mem[adb][7:0]<=dinb[7:0];
        end
        if(byte_enb[1])begin
            mem[adb][15:8]<=dinb[15:8];
        end
    end
end

always@(posedge clkb)begin
    if(reseta)begin
        doutb_reg<=0;
    end
    else begin
        if(ceb)begin
            if(!wreb)begin
                doutb_reg<=mem[adb];
            end
            else begin
                if(byte_enb[0])begin
                    doutb_reg[7:0]<=dinb[7:0];
                end
                else begin
                    doutb_reg[7:0]<=mem[adb][7:0];
                end
                if(byte_enb[1])begin
                    doutb_reg[15:8]<=dinb[15:8];
                end
                else begin
                    doutb_reg[15:8]<=mem[adb][15:8];
                end
            end
        end
    end
end
```



```

        end
    end
end

always@(posedge clk)begin
    if(reset)begin
        doutb<=0;
    end
    else begin
        if(ocb)begin
            doutb<=doutb_reg;
        end
    end
end
endmodule

```

Dual-Port BSRAM with Write-Before-Read Mode and Byte-enable (VHDL)

```

-- Dual-Port BRAM with Byte-wide Write Enable
-- Write First mode
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity gowin_dpb is
    generic(
        DATA_WIDTH : integer := 16;
        ADDRESS_WIDTH : integer := 10
    );
    port (
        dina, dinb : in STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0);
        ada, adb: in STD_LOGIC_VECTOR(ADDRESS_WIDTH - 1
downto 0);
        clka, ocea, cea, wrea, reseta, clk, ocb, ceb, wreb, resetb: in
STD_LOGIC;

```

```

        byte_ena,byte_enb : in STD_LOGIC_VECTOR(1 downto 0);
        douta, doutb : out STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0)
    );
end gowin_dpb;

```

architecture rtl of gowin_dpb is

```

    type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);
    signal mem : mem_type;
    signal douta_reg, doutb_reg :
STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0);
begin

```

```

    process (clka)
    begin
        if (rising_edge(clka)) then
            if(reseta='1')then
                douta <=(others=>'0');
            else
                if(ocea ='1')then
                    douta <= douta_reg;
                end if;
            end if;
        end if;
    end process;

```

```

    process (clka)
    begin
        if (rising_edge(clka)) then
            if(reseta='1')then
                douta_reg <=(others=>'0');
            else
                if(cea ='1')then
                    if(wrea = '0')then
                        douta_reg <= mem(conv_integer(ada));

```

```

                                else
                                    if(byte_ena(0)='1')then
                                        douta_reg(7 downto 0) <= dina(7
downto 0);
                                    else
                                        douta_reg(7 downto 0) <=
mem(conv_integer(ada))(7 downto 0);
                                    end if;
                                    if(byte_ena(1)='1')then
                                        douta_reg(15 downto 8) <= dina(15
downto 8);
                                    else
                                        douta_reg(15 downto 8) <=
mem(conv_integer(ada))(15 downto 8);
                                    end if;
                                end if;
                            end if;
                        end if;
                    end process;

process (clka)
begin
    if (rising_edge(clka)) then
        if(cea ='1'and wrea = '1')then
            if(byte_ena(0)='1')then
                mem(conv_integer(ada))(7 downto 0) <= dina(7
downto 0);
            end if;
            if(byte_ena(1)='1')then
                mem(conv_integer(ada))(15 downto 8) <=
dina(15 downto 8);
            end if;
        end if;
    end if;
end process;

```

```

process (clkb)
begin
    if (rising_edge(clkb)) then
        if(resetb='1')then
            doutb <=(others=>'0');
        else
            if(oceb ='1')then
                doutb <= doutb_reg;
            end if;
        end if;
    end if;
end process;

process (clkb)
begin
    if (rising_edge(clkb)) then
        if(resetb='1')then
            doutb_reg <=(others=>'0');
        else
            if(ceb ='1')then
                if(wreb = '0')then
                    doutb_reg <= mem(conv_integer(adb));
                else
                    if(byte_enb(0)='1')then
                        doutb_reg(7 downto 0) <= dinb(7
downto 0);

                    else
                        doutb_reg(7 downto 0) <=
mem(conv_integer(adb))(7 downto 0);
                    end if;
                    if(byte_enb(1)='1')then
                        doutb_reg(15 downto 8) <= dinb(15
downto 8);

                    else
                        doutb_reg(15 downto 8) <=
mem(conv_integer(adb))(15 downto 8);

```

```

                                end if;
                                end if;
                                end if;
                                end if;
                                end process;

process (clkb)
begin
    if (rising_edge(clkb)) then
        if(ceb ='1'and wreb = '1')then
            if(byte_enb(0)='1')then
                mem(conv_integer(adb))(7 downto 0) <= dinb(7
downto 0);
            end if;
            if(byte_enb(1)='1')then
                mem(conv_integer(adb))(15 downto 8) <=
dinb(15 downto 8);
            end if;
        end if;
    end if;
end process;

end rtl;

```

Semi Dual-Port BSRAM with Byte-enable in Normal Mode (Verilog)

```

// Semi Dual-Port BRAM with Byte-wide Write Enable
// Normal mode
module gowin_sdpb (dout, clka, cea, clkb, oce,ceb, reset, ada, din,
adb, byte_ena);
    output reg[31:0] dout;
    input clka,cea, clkb,ceb,reset,oce;
    input [7:0] ada,adb;
    input [31:0] din;
    input [3:0] byte_ena;

```

```
reg[31:0]mem[2**8-1:0];
reg[31:0] dout_reg;
always@(posedge clka)begin
    if(cea)begin
        if(byte_ena[0])begin
            mem[ada][7:0]<=din[7:0];
        end
        if(byte_ena[1])begin
            mem[ada][15:8]<=din[15:8];
        end
        if(byte_ena[2])begin
            mem[ada][23:16]<=din[23:16];
        end
        if(byte_ena[3])begin
            mem[ada][31:24]<=din[31:24];
        end
    end
end
always@(posedge clk)begin
    if(reset)begin
        dout_reg<=0;
    end
    else begin
        if(ceb)begin
            dout_reg<=mem[adb];
        end
    end
end

always@(posedge clk)begin
    if(reset)begin
        dout<=0;
    end
    else begin
        if(oc)begin
```

```

        dout<=dout_reg;
    end
end
endmodule

```

Semi Dual-Port BSRAM with Byte-enable in Normal Mode (VHDL)

```

-- Semi Dual-Port BRAM with Byte-wide Write Enable
-- Normal mode
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity gowin_sdpb is
    generic(
        ADDRESS_WIDTH : integer := 8;
        DATA_WIDTH : integer := 32
    );
    port (
        din : in STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0);
        ada: in STD_LOGIC_VECTOR(ADDRESS_WIDTH - 1 downto 0);
        clka, cea, clkb, oce,ceb,reset: in STD_LOGIC;
        adb: in STD_LOGIC_VECTOR(ADDRESS_WIDTH - 1 downto 0);
        byte_ena : in STD_LOGIC_VECTOR(3 downto 0);
        dout : out STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0));
end gowin_sdpb;
architecture rtl of gowin_sdpb is
    type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);
    signal mem : mem_type;
    signal dout_reg : STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0);
    begin
        process(clkb)
        begin
            if (rising_edge(clkb)) then
                if (reset='1')then

```

```

        dout <=(others=>'0');
    else
        if(oce = '1')then
            dout <= dout_reg;
        end if;
    end if;
end if;
end process;

process(clkb)
begin
    if (rising_edge(clkb)) then
        if (reset='1')then
            dout_reg <=(others=>'0');
        else
            if(ceb = '1')then
                dout_reg <= mem(conv_integer(adb));
            end if;
        end if;
    end if;
end process;

process (clka)
begin
    if (rising_edge(clka)) then
        if(cea = '1')then
            if(byte_ena(0)='1')then
                mem(conv_integer(ada))(7 downto 0) <= din(7
downto 0);

            end if;

            if(byte_ena(1)='1')then
                mem(conv_integer(ada))(15 downto 8) <=
din(15 downto 8);

            end if;

```



```

                                if(byte_ena(2)=='1')then
                                    mem(conv_integer(ada))(23 downto 16) <=
din(23 downto 16);
                                end if;
                                if(byte_ena(3)=='1')then
                                    mem(conv_integer(ada))(31 downto 24) <=
din(31 downto 24);
                                end if;
                            end if;
                        end if;
                    end process;
                end rtl;

```

8.2 SSRAM

8.2.1 Single-Port SSRAM with Synchronous Read Examples

Single-Port SSRAM with Synchronous Read (Verilog)

```

// Single-Port RAM with Synchronous Read (Distributed RAM)
module gowin_ram16s4(data_out, data_in, addr, clk, wre,rst);
    output reg[3:0]data_out;
    input [3:0]data_in;
    input [3:0]addr;
    input clk,wre,rst;
    reg [3:0] mem [15:0];
    always @(posedge clk)begin
        if ( wre) begin
            mem[addr] <= data_in;
        end
    end
    always @(posedge clk)begin
        if(rst)begin
            data_out<=0;
        end
        else begin
            data_out <= mem[addr];
        end
    end
end

```

```
endmodule
```

Single-Port SSRAM with Synchronous Read (VHDL)

```
-- Single-Port RAM with Synchronous Read (Distributed RAM)
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
use IEEE.std_logic_unsigned.all;
```

```
entity gowin_ram16s4 is
```

```
    generic(
```

```
        DATA_WIDTH : integer := 4;
```

```
        ADDRESS_WIDTH : integer := 4
```

```
    );
```

```
    port (
```

```
        data_in : in STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto 0);
```

```
        addr: in STD_LOGIC_VECTOR(ADDRESS_WIDTH - 1  
downto 0);
```

```
        clk, wre,rst: in STD_LOGIC;
```

```
        data_out : out STD_LOGIC_VECTOR(DATA_WIDTH - 1  
downto 0)
```

```
    );
```

```
end gowin_ram16s4;
```

```
architecture rtl of gowin_ram16s4 is
```

```
    type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
```

```
        STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);
```

```
    signal mem : mem_type;
```

```
begin
```

```
    process (clk)
```

```
    begin
```

```
        if (rising_edge(clk)) then
```

```
            if( wre = '1')then
```

```
                mem(conv_integer(addr)) <= data_in;
```

```

        end if;
    end if;
end process;

process (clk)
begin
    if (rising_edge(clk)) then
        if( rst = '1')then
            data_out <= (others=>'0');
        else
            data_out <= mem(conv_integer(addr));
        end if;
    end if;
end process;
end rtl;

```

8.2.2 Semi Dual-Port SSRAM with Synchronous Read Examples

Semi Dual-Port SSRAM with Synchronous Read (Verilog)

```

// Semi Dual-Port RAM with Synchronous Read (Distributed RAM)
module gowin_ram16sdp4(data_out, data_in, addra, clk, wre,
rst,addrb);
    output reg [3:0]data_out;
    input [3:0]data_in;
    input [3:0] addra ,addrb;
    input clk,wre,rst;

    reg [3:0] mem [15:0];

    always @(posedge clk)begin
        if (wre)begin
            mem[addra] <= data_in;
        end
    end
    always @(posedge clk)begin
        if (rst)begin
            data_out<=0;

```

```

        end
    else begin
        data_out <= mem[addrb];
    end
end
endmodule

```

Semi Dual-Port SSRAM with Synchronous Read (VHDL)

-- Semi Dual-Port RAM with Synchronous Read (Distributed RAM)

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

```

```

entity gowin_ram16sdp4 is
    generic(
        DATA_WIDTH : integer := 4;
        ADDRESS_WIDTH : integer := 4
    );
    port (
        data_in : in STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto
0);
        ada, adb: in STD_LOGIC_VECTOR(ADDRESS_WIDTH - 1
downto 0);
        clk, wre,rst: in STD_LOGIC;
        data_out : out STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0));
end gowin_ram16sdp4;

```

architecture rtl of gowin_ram16sdp4 is

```

    type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
        STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);
    signal mem : mem_type;
begin
    process (clk)
    begin
        if (rising_edge(clk)) then

```

```

        if(wre = '1')then
            mem(conv_integer(ada)) <= data_in;
        end if;
    end if;
end process;

process (clk)
begin
    if (rising_edge(clk)) then
        if(rst = '1')then
            data_out <=(others=>'0');
        else
            data_out <= mem(conv_integer(addr));
        end if;
    end if;
end process;

end rtl;

```

8.3 RAM Initialization

RAM can be initialized using the following methods:

1. Specifies RAM initialization content in HDL source code.
2. Specifies RAM initialization content in external data files.

8.3.1 Specifying RAM Initialization in HDL Source Code

Initial Value Assignment to RAM during its Definition (Verilog)

```

// Initializing Block RAM (Distributed RAM)
module gowin_ram16sdp4 (data_out, data_in, addra, addrb, clk,
ce,rst);
    output reg[15:0]data_out;
    input [15:0]data_in;
    input [2:0]addra, addrb;
    input clk, ce,rst;
    reg [15:0] mem [7:0]={16'h0123,16'h4567,16'h89ab,16'hcdef,
16'h0147, 16'h0258,16'h789a,16'h5678};

    always @(posedge clk)begin

```

```

        if (ce)begin
            mem[addra] <= data_in;
        end
    end
always @(posedge clk)begin
    if (rst)begin
        data_out<=0;
    end
    else begin
        data_out<= mem[addrb];
    end
end
end
endmodule

```

Initial Value Assignment to RAM during its Definition (VHDL)

```

-- Initializing Block RAM (Distributed RAM)
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity gowin_ram16sdp4 is
    generic(
        DATA_WIDTH : integer := 16;
        ADDRESS_WIDTH : integer := 3
    );
    port (
        data_in : in STD_LOGIC_VECTOR(DATA_WIDTH - 1 downto
0);
        addra, addrb: in STD_LOGIC_VECTOR(ADDRESS_WIDTH
- 1 downto 0);
        clk,ce,rst: in STD_LOGIC;
        data_out : out STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0));
    end gowin_ram16sdp4;
architecture rtl of gowin_ram16sdp4 is
    type mem_type is array (2**ADDRESS_WIDTH - 1 downto 0) of
        STD_LOGIC_VECTOR (DATA_WIDTH - 1 downto 0);

```

```

        signal mem :
mem_type:=("0000000100100011","0100010101100111","1000100110101
011","1100110111101111","0000000101000111","0000001001011000","011
1100010011010","0101011001111000");

        signal dout_reg : STD_LOGIC_VECTOR(DATA_WIDTH - 1
downto 0);

    begin
        process (clk)
        begin
            if (rising_edge(clk)) then
                if(ce = '1')then
                    mem(conv_integer(addr_a)) <= data_in;
                end if;
            end if;
        end process;

        process (clk)
        begin
            if (rising_edge(clk)) then
                if(rst = '1')then
                    data_out <= (others=>'0');
                else
                    data_out <= mem(conv_integer(addr_b));
                end if;
            end if;
        end process;
    end rtl;

```

Initial Values Assignment to RAM Using an Initial Block (Verilog)

```

// Initializing Block RAM (Semi Dual-Port Block RAM)
module gowin_sdpb (dout, din, ada, adb, clka,oce, cea, clkb, ceb,
resetb);
    output reg[15:0]dout;
    input [15:0]din;
    input [9:0]ada, adb;
    input clka,oce, cea,clkb, ceb, resetb;
    reg [15:0] mem [1023:0];

```

```

reg[15:0]dout_reg;
integer i;
initial begin
    for (i=0; i<1024; i=i+1)
        mem[i] = i;
end
always @(posedge clka)begin
    if (cea )begin
        mem[ada] <= din;
    end
end

always@(posedge clk)begin
    if(resetb)begin
        dout <= 0;
    end
    else if(oc)begin
        dout <= dout_reg;
    end
end

always@(posedge clk)begin
    if(resetb)begin
        dout_reg <= 0;
    end
    else if(ceb)begin
        dout_reg <= mem[adb];
    end
end
endmodule

```

8.3.2 Specifying RAM Initialization Content in External Data Files

Initial Values Assignment to RAM using readmemh (Verilog)

```

// Initializing Block RAM from external data file
// Hexadecimal data

```



```
module gowin_ram16sdp4 (data_out, data_in, addra, addrb, clk,
ce,rst);
    output reg[15:0]data_out;
    input [15:0]data_in;
    input [2:0]addra, addrb;
    input clk, ce,rst;
    reg [15:0] mem [7:0];

    initial begin
        $readmemh("E:/ram.mi", mem);
    end

    always @(posedge clk)begin
        if (ce)begin
            mem[addra] <= data_in;
        end
    end
    always @(posedge clk)begin
        if (rst)begin
            data_out<=0;
        end
        else begin
            data_out<= mem[addrb];
        end
    end
end
endmodule
```

The ram.mi data is formatted as follows:

```
0123
4567
89ab
cdef
0147
0258
789a
```

5678

Initial Values Assignment to RAM using readmemb (Verilog)

```
// Initializing Block RAM from external data file
// Binary data
module gowin_ram16sdp4 (data_out, data_in, addra, addrb, clk,
ce,rst);
    output reg[15:0]data_out;
    input [15:0]data_in;
    input [2:0]addra, addrb;
    input clk, ce,rst;
    reg [15:0] mem [7:0];

    initial begin
        $readmemb("E:/ram.mi", mem);
    end

    always @(posedge clk)begin
        if (ce)begin
            mem[addra] <= data_in;
        end
    end
    always @(posedge clk)begin
        if (rst)begin
            data_out<=0;
        end
        else begin
            data_out<= mem[addrb];
        end
    end
end
endmodule
```

The ram.mi data is formatted as follows:

```
0000000100100011
0100010110110011
1000100110101011
```

```

1101011010001011
0000000101010101
1111011101110111
1110010110110011
1001100011100000

```

Initial Values Assignment to RAM using readline (VHDL)

```

-- Initializing Block RAM from external data file
-- Binary data
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use std.textio.all;
entity gowin_sdpb is
    port(
        clk : in std_logic;
        we : in std_logic;
        addra,addrb : in std_logic_vector(5 downto 0);
        din : in std_logic_vector(31 downto 0);
        dout : out std_logic_vector(31 downto 0)
    );
end gowin_sdpb;
architecture syn of gowin_sdpb is
    type RamType is array (0 to 63) of bit_vector(31 downto 0);
    impure function InitRam(RamFileName : in string) return
RamType is
        FILE RamFile : text is in RamFileName;
        variable RamFileLine : line;
        variable RAM : RamType;
        begin
            for i in RamType'range loop
                readline(RamFile, RamFileLine);
                read(RamFileLine, RAM(i));
            end loop;
            return RAM;
        end function;

```

```

        signal RAM : RamType := InitRam("E:/ram.mi");
begin
    process(clk)
    begin
        if clk'event and clk = '1' then
            if we = '1' then
                RAM(to_integer(unsigned(addrb))) <= to_bitvector(din);
            end if;
            dout <=
to_stdlogicvector(RAM(to_integer(unsigned(addrb))));
            end if;
        end process;
    end syn;

```

The ram.mi data is formatted as follows:

```

00000001001000111111011101110111
01000101101100110000000100100011
10001001101010111101011010001011
11010110100010111110110110110011
10000001010101011101011010001011
11110111011101111100111011011001
11100101101100111100111011011001
10011000111000001000100110101011
11000001001000111110011101110111
11000101101100111110010110110011
10101001101010110110100110101011
10010110100010111110011101110111
10100001010101011001100011100000
11100111011101111010000101010101
11101101101100110110100110101011
10010000111000001110011101110111
11000010010001101100000100100011
01000101101100101000100110101011
01101001101010111110010110110011
11010110100010111001100011100000
01100001010101011110011101110111

```

```
11001110110110010110000101010101
10011000111000001111011101100111
11000001001000110000000101010101
11000101101100111000100110101011
10101001101010111011011101110111
10010110100010111111000011111111
10100001010101011111000011011011
11100111011101111111000011110011
11101101101100111111000011111111
10010000111111111110010110100011
00000001001000111111000011111111
00000001001000111111011101110111
01000101101100110000000100100011
10001001101010111101011010001011
11010110100010111110110110110011
10000001010101011101011010001011
11110111011101111100111011011001
11100101101100111100111011011001
10011000111000001000100110101011
11000001001000111110011101110111
11000101101100111110010110110011
10101001101010110110100110101011
10010110100010111110011101110111
10100001010101011001100011100000
11100111011101111010000101010101
11101101101100110110100110101011
10010000111000001110011101110111
11000010010001101100000100100011
01000101101100101000100110101011
01101001101010111110010110110011
11010110100010111001100011100000
01100001010101011110011101110111
11001110110110010110000101010101
10011000111000001111011101100111
11000001001000110000000101010101
```

```
11000101101100111000100110101011
10101001101010111011011101110111
10010110100010111111000011111111
10100001010101011111000011011011
11100111011101111111000011110011
11101101101100111111000011111111
10010000111111111110010110100011
00000001001000111111000011111111
```

9_{ROM}

Read-Only Memory (ROM) is very similar to Random-Access Memory (RAM).

9.1 ROM Examples

9.1.1 ROM with Initial Values Assigned at Definition (Verilog)

```
// ROM Inference on array
module gowin_prom(dout, addr,clk,oce, ce,rst);
output reg[31:0]dout;
input [5:0]addr;
input clk, ce,oce,rst;
reg[31:0]dout_reg;
reg [31:0] mem [63:0]={32'h52853fd5,32'h38581bd2, 32'h040d53e4,
32'h22ce7d00,32'hc0b4bf1c,32'hec45e626, 32'hd9d000d9, 32'haacf8574,
32'h8c565693,32'hb19808d0, 32'he073036e,
32'h41b923f6,32'hba17fce1,32'hd4dec5de, 32'ha18ad699, 32'h4a734008,
32'h8f26bdd4,32'hb8d4aab6, 32'hf55e3c77,
32'h41a5d418,32'h5c651d69,32'h445469c3, 32'h2e49668b,
32'hdc1aa05b,
32'h1e1f0f1e,32'h86fd31ef, 32'h73d90e02,
32'hb655bf16,32'hdce89022,32'h5c32ac0e, 32'hba172648, 32'hcebfe4cd,
32'h32853fd5,32'h3858abd2, 32'h04ac53e4,
32'h22ce7d00,32'hc0b4bf1c,32'hec45e626, 32'hd9d000d9, 32'haacf8574,
32'h8c565693,32'hb19808d0, 32'he073036e,
32'h41b923f6,32'hba17fce1,32'hd4dec5de, 32'ha18ad699, 32'h4da34008,
32'h8f26bdd4,32'hb8d4aab6, 32'hf55e3c77,
32'h41a5d418,32'h5c651d69,32'h445469c3, 32'h2e49668b,
32'hdc1aa05b,
32'h1e1f0f1e,32'h86fd31ef, 32'h73d90e02,
32'hb655bf16,32'hdce89022,32'h5c32ac0e, 32'hba172648, 32'hcebfe4cd
```

```

};
always @(posedge clk)begin
    if (rst)begin
        dout<=0;
    end
    else begin
        if(oce)begin
            dout<= dout_reg;
        end
    end
end
always @(posedge clk)begin
    if (rst)begin
        dout_reg<=0;
    end
    else begin
        if(ce)begin
            dout_reg<= mem[addr];
        end
    end
end
endmodule

```

9.1.2 ROM with Initial Values Assigned at Definition (VHDL)

```

-- ROM Inference on array
library ieee;
use ieee.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
ENTITY gowin_prom is
    generic(
        Width : integer := 32;
        Depth : integer := 6
    );
    PORT (clk:IN STD_LOGIC;
          ce,rst:IN STD_LOGIC;

```



```

        addr : STD_LOGIC_VECTOR(Depth-1 DOWNT0 0);
        dout:OUT STD_LOGIC_VECTOR(Width-1 DOWNT0 0)
    );

end gowin_prom;

ARCHITECTURE rtl OF gowin_prom IS
    signal data_out :STD_LOGIC_VECTOR(Width-1 DOWNT0 0);
    TYPE vector_array IS ARRAY(2**Depth-1 DOWNT0 0) OF
    STD_LOGIC_VECTOR(Width-1 DOWNT0 0);
    CONSTANT mem:vector_array:=(
        X"52853fd5",X"38581bd2", X"040d53e4",
        X"22ce7d00",X"c0b4bf1c",X"ec45e626", X"d9d000d9", X"aacf8574",
        X"8c565693",X"b19808d0", X"e073036e",
        X"41b923f6",X"ba17fce1",X"d4dec5de", X"a18ad699", X"4a734008",
        X"8f26bdd4",X"b8d4aab6", X"f55e3c77",
        X"41a5d418",X"5c651d69",X"445469c3", X"2e49668b", X"dc1aa05b",
        X"1e1f0f1e",X"86fd31ef", X"73d90e02",
        X"b655bf16",X"dce89022",X"5c32ac0e", X"ba172648", X"cebfe4cd",
        X"32853fd5",X"3858abd2", X"04ac53e4",
        X"22ce7d00",X"c0b4bf1c",X"ec45e626", X"d9d000d9", X"aacf8574",
        X"8c565693",X"b19808d0", X"e073036e",
        X"41b923f6",X"ba17fce1",X"d4dec5de", X"a18ad699", X"4da34008",
        X"8f26bdd4",X"b8d4aab6", X"f55e3c77",
        X"41a5d418",X"5c651d69",X"445469c3", X"2e49668b", X"dc1aa05b",
        X"1e1f0f1e",X"86fd31ef", X"73d90e02",
        X"b655bf16",X"dce89022",X"5c32ac0e", X"ba172648", X"cebfe4cd"
    );
BEGIN
    PROCESS(clk)
    BEGIN
        IF(clk'EVENT AND clk='1') THEN
            IF(rst='1')THEN
                data_out<=(OTHERS=>'0');
            ELSE
                IF(ce='1') THEN
                    data_out<=mem(conv_integer(addr));
                END IF;
            END IF;
        END IF;
    END PROCESS;
END rtl;

```

```

        END IF;
    END IF;
END IF;
END PROCESS;
PROCESS(clk)
BEGIN
    IF(clk'EVENT AND clk='1') THEN
        IF(rst='1')THEN
            dout<=(OTHERS=>'0');
        ELSE
            IF(ce='1') THEN
                dout<=data_out;
            END IF;
        END IF;
    END IF;
END PROCESS;
END rtl;

```

9.1.3 ROM Implemented Using Case Statement (Verilog)

```

// ROMs Using Block RAM Resources
module gowin_prom(clk,rst,ce,addr,dout);
input clk;
input rst,ce;
input [5:0] addr;
output reg [31:0] dout;
reg [31:0] dout_reg;
always @(posedge clk )begin
    if (rst) begin
        dout_reg <= 0;
    end
    else begin
        if(ce)begin
            case(addr)
                6'h00: dout_reg <= 32'h52853fd5;
                6'h01: dout_reg <= 32'h38581bd2;

```

```
6'h02: dout_reg <= 32'h040d53e4;
6'h03: dout_reg <= 32'h22ce7d00;
6'h04: dout_reg <= 32'h73d90e02;
6'h05: dout_reg <= 32'hc0b4bf1c;
6'h06: dout_reg <= 32'hec45e626;
6'h07: dout_reg <= 32'hd9d000d9;
6'h08: dout_reg <= 32'haacf8574;
6'h09: dout_reg <= 32'hb655bf16;
6'h0a: dout_reg <= 32'h8c565693;
6'h0b: dout_reg <= 32'hb19808d0;
6'h0c: dout_reg <= 32'he073036e;
6'h0d: dout_reg <= 32'h41b923f6;
6'h0e: dout_reg <= 32'hdce89022;
6'h0f: dout_reg <= 32'hba17fce1;
6'h10: dout_reg <= 32'hd4dec5de;
6'h11: dout_reg <= 32'ha18ad699;
6'h12: dout_reg <= 32'h4a734008;
6'h13: dout_reg <= 32'h5c32ac0e;
6'h14: dout_reg <= 32'h8f26bdd4;
6'h15: dout_reg <= 32'hb8d4aab6;
6'h16: dout_reg <= 32'hf55e3c77;
6'h17: dout_reg <= 32'h41a5d418;
6'h18: dout_reg <= 32'hba172648;
6'h19: dout_reg <= 32'h5c651d69;
6'h1a: dout_reg <= 32'h445469c3;
6'h1b: dout_reg <= 32'h2e49668b;
6'h1c: dout_reg <= 32'hdc1aa05b;
6'h1d: dout_reg <= 32'hcebfe4cd;
6'h1e: dout_reg <= 32'h1e1f0f1e;
6'h1f: dout_reg <= 32'h86fd31ef;
6'h20: dout_reg <= 32'h05853fd5;
6'h21: dout_reg <= 32'h38581bd2;
6'h22: dout_reg <= 32'h040d53e4;
6'h23: dout_reg <= 32'h22ce7d00;
6'h24: dout_reg <= 32'h73d90e02;
```

```
        6'h25: dout_reg <= 32'hc0b4bf1c;
        6'h26: dout_reg <= 32'hec45e626;
        6'h27: dout_reg <= 32'hd9d000d9;
        6'h28: dout_reg <= 32'haacf8574;
        6'h29: dout_reg <= 32'hb655bf16;
        6'h2a: dout_reg <= 32'h8c565693;
        6'h2b: dout_reg <= 32'hb19808d0;
        6'h2c: dout_reg <= 32'he073036e;
        6'h2d: dout_reg <= 32'h41b923f6;
        6'h2e: dout_reg <= 32'hdce89022;
        6'h2f: dout_reg <= 32'hba17fce1;
        6'h30: dout_reg <= 32'hd4dec5de;
        6'h31: dout_reg <= 32'ha18ad699;
        6'h32: dout_reg <= 32'h4a734008;
        6'h33: dout_reg <= 32'h5c32ac0e;
        6'h34: dout_reg <= 32'h8f26bdd4;
        6'h35: dout_reg <= 32'hb8d4aab6;
        6'h36: dout_reg <= 32'hc55e3c77;
        6'h37: dout_reg <= 32'h41a5d418;
        6'h38: dout_reg <= 32'hba172648;
        6'h39: dout_reg <= 32'h5a651d69;
        6'h3a: dout_reg <= 32'h445469c3;
        6'h3b: dout_reg <= 32'h2e49668b;
        6'h3c: dout_reg <= 32'hdc1aa05b;
        6'h3d: dout_reg <= 32'hcebfe4cd;
        6'h3e: dout_reg <= 32'h1e1f0f1e;
        6'h3f: dout_reg <= 32'hf6fd31ef;
        default: dout_reg <= 32'h8e9008a6;
    endcase
end
end
always @(posedge clk )begin
    if (rst) begin
        dout <= 0;
```

```

        end
    else begin
        if(ce)begin
            dout<=dout_reg;
        end
    end
end
endmodule

```

9.1.4 ROM Implemented Using Case Statement (VHDL)

-- ROMs Using Block RAM Resources

library ieee;

use ieee.std_logic_1164.all;

ENTITY gowin_prom is

PORT (

clk:IN STD_LOGIC;

ce,rst:IN STD_LOGIC;

addr : STD_LOGIC_VECTOR(5 DOWNT0 0);

dout :OUT STD_LOGIC_VECTOR(31 DOWNT0 0)

);

end gowin_prom;

ARCHITECTURE rtl OF gowin_prom IS

signal dout_reg : STD_LOGIC_VECTOR(31 DOWNT0 0);

BEGIN

PROCESS(clk)

BEGIN

IF(clk'EVENT AND clk='1') THEN

IF(rst='1')THEN

dout<=(OTHERS=>'0');

ELSE

IF(ce='1')THEN

dout <= dout_reg;

END IF;

```
        END IF;
    END IF;
END PROCESS;

PROCESS(clk)
BEGIN
    IF(clk'EVENT AND clk='1') THEN
        IF(rst='1')THEN
            dout_reg<=(OTHERS=>'0');
        ELSE
            IF(ce='1')THEN
                CASE addr IS
                    WHEN b"000000"=> dout_reg <= x"52853fd5";
                    WHEN b"000001"=> dout_reg <= x"38581bd2";
                    WHEN b"000010"=> dout_reg <= x"040d53e4";
                    WHEN b"000011"=> dout_reg <= x"22ce7d00";
                    WHEN b"000100"=> dout_reg <= x"73d90e02";
                    WHEN b"000101"=> dout_reg <= x"c0b4bf1c";
                    WHEN b"000110"=> dout_reg <= x"ec45e626";
                    WHEN b"000111"=> dout_reg <= x"d9d000d9";
                    WHEN b"001000"=> dout_reg <= x"aacf8574";
                    WHEN b"001001"=> dout_reg <= x"b655bf16";
                    WHEN b"001010"=> dout_reg <= x"8c565693";
                    WHEN b"001011"=> dout_reg <= x"b19808d0";
                    WHEN b"001100"=> dout_reg <= x"e073036e";
                    WHEN b"001101"=> dout_reg <= x"41b923f6";
                    WHEN b"001110"=> dout_reg <= x"dce89022";
                    WHEN b"001111"=> dout_reg <= x"ba17fce1";
                    WHEN b"010000"=> dout_reg <= x"d4dec5de";
                    WHEN b"010001"=> dout_reg <= x"a18ad699";
                    WHEN b"010010"=> dout_reg <= x"4a734008";
                    WHEN b"010011"=> dout_reg <= x"5c32ac0e";
                    WHEN b"010100"=> dout_reg <= x"8f26bdd4";
                    WHEN b"010101"=> dout_reg <= x"b8d4aab6";
                    WHEN b"010110"=> dout_reg <= x"f55e3c77";
```

```
WHEN b"010111"=> dout_reg <= x"41a5d418";
WHEN b"011000"=> dout_reg <= x"ba172648";
WHEN b"011001"=> dout_reg <= x"5c651d69";
WHEN b"011010"=> dout_reg <= x"445469c3";
WHEN b"011011"=> dout_reg <= x"2e49668b";
WHEN b"011100"=> dout_reg <= x"dc1aa05b";
WHEN b"011101"=> dout_reg <= x"cebfe4cd";
WHEN b"011110"=> dout_reg <= x"1e1f0f1e";
WHEN b"011111"=> dout_reg <= x"86fd31ef";
WHEN b"100000"=> dout_reg <= x"fa853fd5";
WHEN b"100001"=> dout_reg <= x"38581bd2";
WHEN b"100010"=> dout_reg <= x"f40d53e4";
WHEN b"100011"=> dout_reg <= x"22ce7d00";
WHEN b"100100"=> dout_reg <= x"73d90e02";
WHEN b"100101"=> dout_reg <= x"c0b4bf1c";
WHEN b"100110"=> dout_reg <= x"ec45e626";
WHEN b"100111"=> dout_reg <= x"d9d000d9";
WHEN b"101000"=> dout_reg <= x"aacf8574";
WHEN b"101001"=> dout_reg <= x"b655bf16";
WHEN b"101010"=> dout_reg <= x"8c565693";
WHEN b"101011"=> dout_reg <= x"b19808d0";
WHEN b"101100"=> dout_reg <= x"e073036e";
WHEN b"101101"=> dout_reg <= x"41b923f6";
WHEN b"101110"=> dout_reg <= x"dce89022";
WHEN b"101111"=> dout_reg <= x"ba17fce1";
WHEN b"110000"=> dout_reg <= x"d4dec5de";
WHEN b"110001"=> dout_reg <= x"a18ad699";
WHEN b"110010"=> dout_reg <= x"fa734008";
WHEN b"110011"=> dout_reg <= x"cc32ac0e";
WHEN b"110100"=> dout_reg <= x"af26bdd4";
WHEN b"110101"=> dout_reg <= x"b8d4aab6";
WHEN b"110110"=> dout_reg <= x"f55e3c77";
WHEN b"110111"=> dout_reg <= x"41a5d418";
WHEN b"111000"=> dout_reg <= x"ba172648";
WHEN b"111001"=> dout_reg <= x"5c651d69";
```

```

        WHEN b"111010"=> dout_reg <= x"445469c3";
        WHEN b"111011"=> dout_reg <= x"2e49668b";
        WHEN b"111100"=> dout_reg <= x"dc1aa05b";
        WHEN b"111101"=> dout_reg <= x"cebfe4cd";
        WHEN b"111110"=> dout_reg <= x"1e1f0f1e";
        WHEN b"111111"=> dout_reg <= x"86fd31ef";
        WHEN OTHERS => dout_reg <= x"8e9008a6";
    END CASE;
END IF;
END IF;
END IF;
END PROCESS;
END rtl;

```

9.1.5 ROM with Initial Values Assigned Using Initial Block (Verilog)

```

// ROM Inference on array
module gowin_prom(dout, addr,clk, ce,rst);
output reg[9:0]dout;
input [9:0]addr;
input clk, ce,rst;
reg [9:0] mem [1023:0];
integer i;
initial begin
    for (i=0; i<1023; i=i+1)
        mem[i] = i;
end
always @(posedge clk)begin
    if (rst)begin
        dout<=0;
    end
    else begin
        if(ce)begin
            dout<= mem[addr];
        end
    end
end
end

```



```

end
endmodule

```

9.1.6 ROM with Initial Values Assigned Using readmemh (Verilog)

```

// ROM Inference on array
module gowin_prom(dout,addr, clk, ce,rst);
output reg[31:0]dout;
input [5:0]addr;
input clk, ce,rst;
reg [31:0] mem [63:0];

initial begin
    $readmemh("E:/ram.mi", mem);
end

always @(posedge clk)begin
    if (rst)begin
        dout<=0;
    end
    else begin
        if(ce)begin
            dout<= mem[addr];
        end
    end
end
endmodule

```

The ram.mi data is written as follows:

```

52853fd5
38581bd2
040d53e4
22ce7d00
c0b4bf1c
ec45e626
d9d000d9
aacf8574

```

8c565693
b19808d0
e073036e
41b923f6
ba17fce1
d4dec5de
a18ad699
4a734008
8f26bdd4
b8d4aab6
f55e3c77
41a5d418
5c651d69
445469c3
2e49668b
dc1aa05b
1e1f0f1e
86fd31ef
73d90e02
b655bf16
dce89022
5c32ac0e
ba172648
cebfe4cd
32853fd5
3858abd2
04ac53e4
22ce7d00
c0b4bf1c
ec45e626
d9d000d9
aacf8574
8c565693
b19808d0
e073036e

```
41b923f6
ba17fce1
d4dec5de
a18ad699
4da34008
8f26bdd4
b8d4aab6
f55e3c77
41a5d418
5c651d69
445469c3
2e49668b
dc1aa05b
1e1f0f1e
86fd31ef
73d90e02
b655bf16
dce89022
5c32ac0e
ba172648
cebfe4cd
```

9.1.7 ROM with Initial Values Assigned Using readmemb (Verilog)

```
// ROM Inference on array
module gowin_prom(dout,addr, clk, ce,rst);
output reg[31:0]dout;
input [5:0]addr;
input clk, ce,rst;
reg [31:0] mem [63:0];

initial begin
    $readmemb("E:/ram.mi", mem);
end

always @(posedge clk)begin
```

```

        if (rst)begin
            dout<=0;
        end
        else begin
            if(ce)begin
                dout<= mem[addr];
            end
        end
    end
end
endmodule

```

The ram.mi data is written as follows:

```

00000001001000111111011101110111
01000101101100110000000100100011
10001001101010111101011010001011
11010110100010111110110110110011
10000001010101011101011010001011
11110111011101111100111011011001
11100101101100111100111011011001
10011000111000001000100110101011
11000001001000111110011101110111
11000101101100111110010110110011
10101001101010110110100110101011
10010110100010111110011101110111
10100001010101011001100011100000
11100111011101111010000101010101
11101101101100110110100110101011
10010000111000001110011101110111
11000010010001101100000100100011
01000101101100101000100110101011
01101001101010111110010110110011
11010110100010111001100011100000
01100001010101011110011101110111
11001110110110010110000101010101
10011000111000001111011101100111

```

```
11000001001000110000000101010101
11000101101100111000100110101011
1010100110101011101101110110111
10010110100010111111000011111111
10100001010101011111000011011011
11100111011011111111000011110011
11101101101100111111000011111111
10010000111111111110010110100011
00000001001000111111000011111111
00000001001000111111011101110111
01000101101100110000000100100011
10001001101010111101011010001011
11010110100010111110110110110011
10000001010101011101011010001011
11110111011101111100111011011001
11100101101100111100111011011001
10011000111000001000100110101011
11000001001000111110011101110111
11000101101100111110010110110011
10101001101010110110100110101011
10010110100010111110011101110111
10100001010101011001100011100000
11100111011101111010000101010101
11101101101100110110100110101011
10010000111000001110011101110111
11000010010001101100000100100011
01000101101100101000100110101011
01101001101010111110010110110011
11010110100010111001100011100000
01100001010101011110011101110111
11001110110110010110000101010101
10011000111000001111011101100111
11000001001000110000000101010101
11000101101100111000100110101011
10101001101010111011011101110111
```

```

10010110100010111111000011111111
10100001010101011111000011011011
11100111011101111111000011110011
11101101101100111111000011111111
10010000111111111110010110100011
00000001001000111111000011111111

```

9.1.8 ROM with Initial Values Assigned Using readline (VHDL)

```

-- ROM Inference on array
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use std.textio.all;
entity gowin_prom is
    port(
        clk : in std_logic;
        ce : in std_logic;
        addr : in std_logic_vector(5 downto 0);
        dout : out std_logic_vector(31 downto 0)
    );
end gowin_prom;
architecture syn of gowin_prom is
    type RamType is array (0 to 63) of bit_vector(31 downto 0);
    impure function InitRam(RamFileName : in string) return
RamType is
        FILE RamFile : text is in RamFileName;
        variable RamFileLine : line;
        variable RAM : RamType;
        begin
            for i in RamType'range loop
                readline(RamFile, RamFileLine);
                read(RamFileLine, RAM(i));
            end loop;
            return RAM;
        end function;
    signal RAM : RamType := InitRam("E:/ram.mi");

```

```

begin
process(clk)
begin
    if clk'event and clk = '1' then
        if ce = '1' then
            dout <=
to_stdlogicvector(RAM(to_integer(unsigned(addr))));
        end if;
    end if;
end process;
end syn;

```

The ram.mi data is written as follows:

```

00000001001000111111011101110111
01000101101100110000000100100011
10001001101010111101011010001011
11010110100010111110110110110011
10000001010101011101011010001011
11110111011101111100111011011001
11100101101100111100111011011001
10011000111000001000100110101011
11000001001000111110011101110111
11000101101100111110010110110011
10101001101010110110100110101011
10010110100010111110011101110111
10100001010101011001100011100000
11100111011101111010000101010101
11101101101100110110100110101011
10010000111000001110011101110111
11000010010001101100000100100011
01000101101100101000100110101011
01101001101010111110010110110011
11010110100010111001100011100000
01100001010101011110011101110111
11001110110110010110000101010101
10011000111000001111011101100111

```

```
11000001001000110000000101010101
11000101101100111000100110101011
1010100110101011101101110110111
10010110100010111111000011111111
10100001010101011111000011011011
11100111011011111111000011110011
11101101101100111111000011111111
10010000111111111110010110100011
00000001001000111111000011111111
00000001001000111111011101110111
01000101101100110000000100100011
10001001101010111101011010001011
11010110100010111110110110110011
10000001010101011101011010001011
11110111011101111100111011011001
11100101101100111100111011011001
10011000111000001000100110101011
11000001001000111110011101110111
11000101101100111110010110110011
10101001101010110110100110101011
10010110100010111110011101110111
10100001010101011001100011100000
11100111011101111010000101010101
11101101101100110110100110101011
10010000111000001110011101110111
11000010010001101100000100100011
01000101101100101000100110101011
01101001101010111110010110110011
11010110100010111001100011100000
01100001010101011110011101110111
11001110110110010110000101010101
10011000111000001111011101100111
11000001001000110000000101010101
11000101101100111000100110101011
10101001101010111011011101110111
```



```
10010110100010111111000011111111
10100001010101011111000011011011
11100111011101111111000011110011
11101101101100111111000011111111
1001000011111111110010110100011
00000001001000111111000011111111
```

10_{DSP}

10.1 Pre-adder

10.1.1 Static Pre-adder/subtractor Operation Examples

Static Pre-adder Followed by Multiplier (Verilog)

```
// Static pre-addition followed by multiplier
// device:GW1N/GW2A
module gowin_padd18(clk,rst,ce,a,b,d,dout);
input [15:0]a;
input [15:0]b;
input [15:0]d;
input clk;
input ce,rst;
output reg [31:0]dout;

reg [15:0]a_reg;
reg [15:0]b_reg;
reg [15:0]d_reg;

always@(posedge clk)begin
    if(rst)begin
        a_reg<=0;
        b_reg<=0;
        d_reg<=0;
    end
    else begin
```

```

        if(ce)begin
            a_reg<=a;
            b_reg<=b;
            d_reg<=d;
        end
    end
end

always@(posedge clk)begin
    if(rst)begin
        dout<=0;
    end
    else begin
        if(ce)begin
            dout<=(a_reg+d_reg)*b_reg;
        end
    end
end
endmodule

```

Static Pre-subtractor Followed by Multiplier (VHDL)

```

-- Static pre-subtract followed by multiplier
-- device:GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity gowin_multalu27x18 is
    generic(
        a_width : integer := 26;
        b_width : integer := 17;
        d_width : integer := 26;
        dout_width : integer := 44
    );
    port (
        dout: out signed (dout_width-1 downto 0);

```

```

        a : in signed (a_width-1 downto 0);
        b : in signed (b_width-1 downto 0);
        d : in signed (d_width-1 downto 0);
        clk: in std_logic;
        ce,rst: in std_logic
    );
end gowin_multalu27x18;
architecture Behavioral of gowin_multalu27x18 is
    signal ad_add:signed (a_width  downto 0);
    signal a_reg : signed (a_width-1 downto 0);
    signal b_reg : signed (b_width-1 downto 0);
    signal d_reg : signed (d_width-1 downto 0);
begin
    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                a_reg<=(others=>'0');
                b_reg<=(others=>'0');
                d_reg<=(others=>'0');
            else
                if(ce='1')then
                    a_reg<=a;
                    b_reg<=b;
                    d_reg<=d;
                end if;
            end if;
        end if;
    end process;

    ad_add<=resize(a_reg,27)-resize(d_reg,27);
    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                dout<=(others=>'0');

```

```

        else
            if(ce='1')then
                dout<=ad_add*b_reg;
            end if;
        end if;
    end if;
end process;
end Behavioral;

```

Static Pre-adder Followed by Multiplier and Post-adder (Verilog)

```

// Static pre-adder followed by multiplier and post-adder
// device: GW5A
module gowin_multalu27x18(clk,rst,ce,a,b,c,d,dout);
input signed[25:0]a;
input signed[17:0]b;
input signed[25:0]d;
input signed[47:0]c;
input clk;
input ce,rst;
output reg signed[47:0]dout;
reg signed[43:0]mout;
reg signed[25:0]a_reg;
reg signed[17:0]b_reg;
reg signed[25:0]d_reg;
reg signed[47:0]c_reg;

always@(posedge clk)begin
    if(rst)begin
        a_reg<=0;
        b_reg<=0;
        c_reg<=0;
        d_reg<=0;
    end
    else begin
        if(ce)begin
            a_reg<=a;

```

```

        b_reg<=b;
        c_reg<=c;
        d_reg<=d;
    end
end
end

always@(posedge clk)begin
    if(rst)begin
        dout<=0;
        mout<=0;
    end
    else begin
        if(ce)begin
            mout<=(a_reg+d_reg)*b_reg;
            dout<=mout+c_reg;
        end
    end
end
end
endmodule

```

Static Pre-adder Followed by Multiplier and Post-adder (VHDL)

```

-- Static pre-adder followed by multiplier and post-adder
-- device: GW1N/GW2A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity gowin_padd18 is
    generic(
        a_width : integer := 17;
        b_width : integer := 17;
        d_width : integer := 17;
        dout_width : integer := 48
    );
    port (

```

```

        dout: out unsigned (dout_width-1 downto 0);
        a : in unsigned (a_width-1 downto 0);
        b : in unsigned (b_width-1 downto 0);
        c : in unsigned (dout_width-1 downto 0);
        d : in unsigned (d_width-1 downto 0);
        clk: in std_logic;
        ce,rst: in std_logic
    );
end gowin_padd18;
architecture Behavioral of gowin_padd18 is
    signal ad_add: unsigned (a_width  downto 0);
    signal a_reg : unsigned (a_width-1 downto 0);
    signal b_reg : unsigned (b_width-1 downto 0);
    signal c_reg : unsigned (dout_width-1 downto 0);
    signal d_reg : unsigned (d_width-1 downto 0);
begin
    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                a_reg<=(others=>'0');
                b_reg<=(others=>'0');
                c_reg<=(others=>'0');
                d_reg<=(others=>'0');
            else
                if(ce='1')then
                    a_reg<=a;
                    b_reg<=b;
                    c_reg<=c;
                    d_reg<=d;
                end if;
            end if;
        end if;
    end process;

    ad_add<=resize(a_reg,18)-resize(d_reg,18);

```

```

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            dout<=(others=>'0');
        else
            if(ce='1')then
                dout<=ad_add*b_reg+c_reg;
            end if;
        end if;
    end if;
end process;
end Behavioral;

```

10.1.2 Dynamic Pre-adder/subtractor Operation Examples

Dynamic Pre-adder/subtractor Followed by Multiplier (Verilog)

```

// Pre-add/subtract select with Dynamic control
// device:GW5A
module gowin_multalu27x18(clk,ce,reset,a,b,d,psel,dout);
    input signed [15:0]a;
    input signed [15:0]b;
    input signed [15:0]d;
    input psel;
    input [1:0]clk,ce,reset;
    output reg signed [31:0]dout;
    reg signed [31:0]preg;

    reg signed [15:0]a_reg;
    reg signed [15:0]b_reg;
    reg signed [15:0]d_reg;
    always@(posedge clk[0])begin
        if(reset[0])begin
            a_reg<=0;
            b_reg<=0;
            d_reg<=0;
        end
    end

```



```

        else begin
            if(ce[0])begin
                a_reg<=a;
                b_reg<=b;
                d_reg<=d;
            end
        end
    end
end

always@(posedge clk[1])begin
    if(reset[1])begin
        preg<=0;
    end
    else begin
        if(ce[1])begin
            preg<=psel ? (a_reg-d_reg)*b_reg :
(a_reg+d_reg)*b_reg;
        end
    end
end

always@(posedge clk[1])begin
    if(reset[1])begin
        dout<=0;
    end
    else begin
        if(ce[1])begin
            dout<=preg;
        end
    end
end
endmodule

```

Dynamic Pre-adder/subtractor Followed by Multiplier (VHDL)

```

-- Pre-add/subtract select with Dynamic control
-- device:GW5A
library IEEE;

```

```

use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity gowin_multalu27x18 is
    generic(
        a_width : integer := 16;
        b_width : integer := 16;
        d_width : integer := 16;
        dout_width : integer := 33
    );
    port (
        dout: out signed (dout_width-1 downto 0);
        a : in signed (a_width-1 downto 0);
        b : in signed (b_width-1 downto 0);
        d : in signed (d_width-1 downto 0);
        psel : in std_logic;
        clk,ce,reset:in signed (1 downto 0)
    );
end gowin_multalu27x18;
architecture Behavioral of gowin_multalu27x18 is
    signal preg:signed (dout_width-1 downto 0);
    signal a_reg : signed (a_width-1 downto 0);
    signal b_reg : signed (b_width-1 downto 0);
    signal d_reg : signed (d_width-1 downto 0);
begin
    process(clk(0))begin
        if(rising_edge(clk(0)))then
            if(reset(0)='1')then
                a_reg<=(others=>'0');
                b_reg<=(others=>'0');
                d_reg<=(others=>'0');
            else
                if(ce(0)='1')then
                    a_reg<=a;
                    b_reg<=b;
                    d_reg<=d;
                end if;
            end if;
        end if;
    end process;
end Behavioral;

```

```

        end if;
    end if;
end if;
end process;

process(clk(1))begin
    if(rising_edge(clk(1)))then
        if(reset(1)='1')then
            preg<=(others=>'0');
        else
            if(ce(1)='1')then
                if(psel='0')then
                    preg<=((a_reg(a_width-1)&a_reg) +
(d_reg(d_width-1) &d_reg))*b_reg;
                else
                    preg<=((a_reg(a_width-1)&a_reg) -
(d_reg(d_width-1) &d_reg))*b_reg;
                end if;
            end if;
        end if;
    end if;
end if;
end process;

process(clk(1))begin
    if(rising_edge(clk(1)))then
        if(reset(1)='1')then
            dout<=(others=>'0');
        else
            if(ce(1)='1')then
                dout<=preg;
            end if;
        end if;
    end if;
end process;
end Behavioral;

```

**Dynamic Pre-adder/subtractor Followed by Multiplier and Adder
(Verilog)**

// Dynamic pre-addition/subtraction followed by multiplier and followed
by adder

// device: GW5A

module gowin_multalu27x18(clk,ce,reset,a,b,c,d,psel,dout);

input signed [25:0]a;

input signed [17:0]b;

input signed [47:0]c;

input signed [25:0]d;

input psel;

input [1:0]clk,ce,reset;

output reg signed [47:0]dout;

reg signed [43:0]preg;

reg signed [25:0]a_reg;

reg signed [17:0]b_reg;

reg signed [47:0]c_reg;

reg signed [25:0]d_reg;

always@(posedge clk[0])begin

if(reset[0])begin

a_reg<=0;

b_reg<=0;

c_reg<=0;

d_reg<=0;

end

else begin

if(ce[0])begin

a_reg<=a;

b_reg<=b;

c_reg<=c;

d_reg<=d;

end

end

end

```

always@(posedge clk[1])begin
    if(reset[1])begin
        preg<=0;
    end
    else begin
        if(ce[1])begin
            preg<=psel ? (a_reg-d_reg)*b_reg :
(a_reg+d_reg)*b_reg;
        end
    end
end
end

```

```

always@(posedge clk[1])begin
    if(reset[1])begin
        dout<=0;
    end
    else begin
        if(ce[1])begin
            dout<=preg+c;
        end
    end
end
endmodule

```

Dynamic Pre-adder/subtractor Followed by Multiplier and Adder (VHDL)

--Dynamic pre-addition/subtraction of Signed data followed by multiplier

-- device: GW5A

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

entity gowin_multalu27x18 is

generic(

```

    a_width : integer := 26;
    b_width : integer := 18;
    c_width : integer := 48;
    d_width : integer := 26;
    dout_width : integer := 48
);
port (
    dout: out signed (dout_width-1 downto 0);
    a : in signed (a_width-1 downto 0);
    b : in signed (b_width-1 downto 0);
    c : in signed (c_width-1 downto 0);
    d : in signed (d_width-1 downto 0);
    psel : in std_logic;
    clk,ce,reset:in signed (1 downto 0)
);
end gowin_multalu27x18;
architecture Behavioral of gowin_multalu27x18 is
    signal preg:signed (a_width+b_width downto 0);
    signal a_reg : signed (a_width-1 downto 0);
    signal b_reg : signed (b_width-1 downto 0);
    signal c_reg : signed (c_width-1 downto 0);
    signal d_reg : signed (d_width-1 downto 0);
begin
    process(clk(0))begin
        if(rising_edge(clk(0)))then
            if(reset(0)='1')then
                a_reg<=(others=>'0');
                b_reg<=(others=>'0');
                c_reg<=(others=>'0');
                d_reg<=(others=>'0');
            else
                if(ce(0)='1')then
                    a_reg<=a;
                    b_reg<=b;
                    c_reg<=c;

```

```
        d_reg<=d;
    end if;
end if;
end if;
end process;

process(clk(1))begin
    if(rising_edge(clk(1)))then
        if(reset(1)='1')then
            preg<=(others=>'0');
        else
            if(ce(1)='1')then
                if(psel='0')then
                    preg<=((a_reg(a_width-1)&a_reg) +
(d_reg(d_width-1) &d_reg))*b_reg;
                else
                    preg<=((a_reg(a_width-1)&a_reg) -
(d_reg(d_width-1) &d_reg))*b_reg;
                end if;
            end if;
        end if;
    end if;
end process;

process(clk(1))begin
    if(rising_edge(clk(1)))then
        if(reset(1)='1')then
            dout<=(others=>'0');
        else
            if(ce(1)='1')then
                dout<=preg+c;
            end if;
        end if;
    end if;
end process;
```

end Behavioral;

10.2 Multiplier

10.2.1 Multiplier Examples

Unsigned 18X27-bit Multiplier (Verilog)

```
// Unsigned 18X27 bit Multiplier
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW1N/GW2A
module gowin_multalu36x18(a,b,clk,ce,rst,out);
input [26:0]a;
input [17:0]b;
input clk,ce,rst;
output [44:0]out;
reg [26:0]a_reg;
reg [17:0]b_reg;
reg [44:0]pp_reg,out_reg;
always@(posedge clk or posedge rst)begin
    if (rst)begin
        a_reg<=0;
        b_reg<=0;
    end
    else begin
        if(ce)begin
            a_reg<=a;
            b_reg<=b;
        end
    end
end
always@(posedge clk or posedge rst)begin
    if (rst)begin
        pp_reg<=0;
    end
    else begin
        if(ce)begin
```



```

        pp_reg<=a_reg*b_reg;
    end
end
end
always@(posedge clk or posedge rst)begin
    if (rst)begin
        out_reg<=0;
    end
    else begin
        if(ce)begin
            out_reg<=pp_reg;
        end
    end
end
end

assign out=out_reg;
endmodule

```

Unsigned 18X27-bit Multiplier (VHDL)

```

-- Unsigned 18x27 bit Multiplier
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity gowin_mult27x36 is
    generic(
        a_width : integer := 27;
        b_width : integer := 18;
        dout_width : integer := 45
    );
    port (
        dout: out unsigned (dout_width-1 downto 0);
        a : in unsigned (a_width-1 downto 0);

```

```

        b : in unsigned (b_width-1 downto 0);
        clk,ce,rst:in std_logic
    );
end gowin_mult27x36;
architecture Behavioral of gowin_mult27x36 is
    signal a_reg : unsigned (a_width-1 downto 0);
    signal b_reg : unsigned (b_width-1 downto 0);
    signal pp_reg,out_reg:unsigned (dout_width-1 downto 0);
begin
    process(clk,rst)begin
        if(rst='1')then
            a_reg<=(others=>'0');
            b_reg<=(others=>'0');
        else
            if(rising_edge(clk))then
                if(ce='1')then
                    a_reg<=a;
                    b_reg<=b;
                end if;
            end if;
        end if;
    end process;
    process(clk,rst)begin
        if(rst='1')then
            pp_reg<=(others=>'0');
        else
            if(rising_edge(clk))then
                if(ce='1')then
                    pp_reg<=a_reg*b_reg;
                end if;
            end if;
        end if;
    end process;
    process(clk,rst)begin
        if(rst='1')then

```

```

        out_reg<=(others=>'0');
    else
        if(rising_edge(clk))then
            if(ce='1')then
                out_reg<=pp_reg;
            end if;
        end if;
    end if;
end process;
dout<=out_reg;
end Behavioral;

```

Signed 18X18-bit Multiplier (Verilog)

```

// Signed 18x18 bit Multiplier
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW1N/GW2A
module gowin_mult18x18(a,b,clk,ce,rst,out);
input signed[17:0]a;
input signed[17:0]b;
input clk,ce,rst;
output signed[35:0]out;
reg signed[17:0]a_reg;
reg signed[17:0]b_reg;
reg signed[35:0]pp_reg,out_reg;
always@(posedge clk or posedge rst)begin
    if (rst)begin
        a_reg<=0;
        b_reg<=0;
    end
    else begin
        if(ce)begin
            a_reg<=a;
            b_reg<=b;
        end
    end
end
end

```

```

end
always@(posedge clk or posedge rst)begin
    if (rst)begin
        pp_reg<=0;
    end
    else begin
        if(ce)begin
            pp_reg<=a_reg*b_reg;
        end
    end
end
end
always@(posedge clk or posedge rst)begin
    if (rst)begin
        out_reg<=0;
    end
    else begin
        if(ce)begin
            out_reg<=pp_reg;
        end
    end
end
end

assign out=out_reg;
endmodule

```

Signed 18X18-bit Multiplier (VHDL)

```

-- Signed 18x18 bit Multiplier
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity gowin_multalu27x18 is
    generic(

```

```

        a_width : integer := 18;
        b_width : integer := 18;
        dout_width : integer := 36
    );
    port (
        dout: out signed (dout_width-1 downto 0);
        a : in signed (a_width-1 downto 0);
        b : in signed (b_width-1 downto 0);
        clk,ce,rst:in signed (1 downto 0)
    );
end gowin_multalu27x18;
architecture Behavioral of gowin_multalu27x18 is
    signal a_reg : signed (a_width-1 downto 0);
    signal b_reg : signed (b_width-1 downto 0);
    signal pp_reg,out_reg: signed (dout_width-1 downto 0);
begin
    process(clk(0),rst(0))begin
        if(rst(0)='1')then
            a_reg<=(others=>'0');
            b_reg<=(others=>'0');
        else
            if(rising_edge(clk(0)))then
                if(ce(0)='1')then
                    a_reg<=a;
                    b_reg<=b;
                end if;
            end if;
        end if;
    end process;

    process(clk(1),rst(1))begin
        if(rst(1)='1')then
            pp_reg<=(others=>'0');
        else
            if(rising_edge(clk(1)))then

```

```

        if(ce(1)='1')then
            pp_reg<=a_reg*b_reg;
        end if;
    end if;
end if;
end process;

process(clk(1),rst(1))begin
    if(rst(1)='1')then
        out_reg<=(others=>'0');
    else
        if(rising_edge(clk(1)))then
            if(ce(1)='1')then
                out_reg<=pp_reg;
            end if;
        end if;
    end if;
end process;
dout<=out_reg;
end Behavioral;

```

10.3 Multiply-Accumulator (MAC)

10.3.1 Static Multiply-add/subtract Examples

Static Multiply-accumulate of Two Multipliers (Verilog)

```

// Static multiply-accumulate of unsigned 12x12 bit multiplier
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW1N/GW2A
module gowin_multaddalu18x18 (clk,ce,rst,a,b,d0,d1,dout);
    input clk,ce,rst;
    input [11:0]a;
    input [11:0]b;
    input [11:0]d0;
    input [11:0]d1;
    output reg [24:0]dout;

```

```
reg [11:0]a_reg;
reg [11:0]b_reg;
reg [11:0]d0_reg;
reg [11:0]d1_reg;
reg [23:0]preg0,preg1;
always@(posedge clk)begin
    if(rst)begin
        a_reg<=0;
        b_reg<=0;
        d0_reg<=0;
        d1_reg<=0;
    end
    else begin
        if(ce)begin
            a_reg<=a;
            b_reg<=b;
            d0_reg<=d0;
            d1_reg<=d1;
        end
    end
end

always@(posedge clk)begin
    if(rst)begin
        dout<=0;
        preg0<=0;
        preg1<=0;
    end
    else begin
        if(ce)begin
            dout<=preg0+preg1;
            preg0<=a_reg*b_reg;
            preg1<=d0_reg*d1_reg;
        end
    end
end
```

```

        end
    end
endmodule

```

Static Multiplication and Subtraction of Multipliers (VHDL)

```

-- Static multiplication and subtraction of 2 multipliers
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity gowin_multalu27x18 is
    generic(
        a_width : integer := 26;
        b_width : integer := 17;
        dout_width : integer := 43
    );
    port (
        dout: out unsigned (dout_width-1 downto 0);
        a,d0 : in unsigned (a_width-1 downto 0);
        b,d1 : in unsigned (b_width-1 downto 0);
        clk,ce,rst: in std_logic
    );
end gowin_multalu27x18;

architecture Behavioral of gowin_multalu27x18 is
    signal mult1,mult2 : unsigned (dout_width-1 downto 0);
    signal a_reg,d0_reg : unsigned (a_width-1 downto 0);
    signal b_reg,d1_reg : unsigned (b_width-1 downto 0);
begin
    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                a_reg<=(others=>'0');
                b_reg<=(others=>'0');

```



```

        d0_reg<=(others=>'0');
        d1_reg<=(others=>'0');
    else
        if(ce='1')then
            a_reg<=a;
            b_reg<=b;
            d0_reg<=d0;
            d1_reg<=d1;
        end if;
    end if;
end if;
end process;

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            mult1<=(others=>'0');
            mult2<=(others=>'0');
            dout<=(others=>'0');
        else
            if(ce='1')then
                mult1<=a_reg*b_reg;
                mult2<=d0_reg*d1_reg;
                dout<=mult1-mult2;
            end if;
        end if;
    end if;
end process;
end Behavioral;

```

Static Multiplication and Addition of Multipliers and Addends (Verilog)

```

// Static multiplication and addition of multipliers and addends
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW1N/GW2A

```

```
module gowin_multaddalu18x18(a,b,c,clk,ce,rst,out);
input [11:0]a;
input [11:0]b;
input [46:0]c;
input  clk,ce,rst;
output [46:0]out;
reg [11:0]a_reg;
reg [11:0]b_reg;
reg [46:0]c_reg;

reg [46:0]pp_reg,out_reg;

always@(posedge clk)begin
    if (rst)begin
        a_reg<=0;
        b_reg<=0;
        c_reg<=0;
    end
    else begin
        if(ce)begin
            a_reg<=a;
            b_reg<=b;
            c_reg<=c;
        end
    end
end

always@(posedge clk)begin
    if (rst)begin
        pp_reg<=0;
    end
    else begin
        if(ce)begin
            pp_reg<=a_reg*b_reg;
        end
    end
end
```

```

end
always@(posedge clk)begin
    if (rst)begin
        out_reg<=0;
    end
    else begin
        if(ce)begin
            out_reg<= pp_reg + c_reg ;
        end
    end
end
end

assign out=out_reg;
endmodule

```

Static Multiplication and Subtraction of Multipliers and Addends (VHDL)

```

-- Static multiplication and subtraction of multipliers and addends
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity gowin_multalu27x18 is
    generic(
        a_width : integer := 12;
        b_width : integer := 12;
        c_width : integer := 47;
        dout_width : integer := 47
    );
    port (
        dout: out std_logic_vector (dout_width-1 downto 0);
        a : in std_logic_vector (a_width-1 downto 0);
        b : in std_logic_vector (b_width-1 downto 0);

```

```

        c : in std_logic_vector (c_width-1 downto 0);
        clk,ce,rst:in std_logic
    );
end gowin_multalu27x18;
architecture Behavioral of gowin_multalu27x18 is
    signal a_reg : std_logic_vector (a_width-1 downto 0);
    signal b_reg : std_logic_vector (b_width-1 downto 0);
    signal c_reg : std_logic_vector (c_width-1 downto 0);
    signal pp_reg: std_logic_vector (a_width+b_width-1 downto 0);
    signal out_reg: std_logic_vector (dout_width-1 downto 0);
begin

    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                a_reg<=(others=>'0');
                b_reg<=(others=>'0');
                c_reg<=(others=>'0');
            else
                if(ce='1')then
                    a_reg<=a;
                    b_reg<=b;
                    c_reg<=c;
                end if;
            end if;
        end if;
    end process;
    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                pp_reg<=(others=>'0');
            else
                if(ce='1')then
                    pp_reg<=a_reg*b_reg;
                end if;
            end if;
        end if;
    end process;
end architecture Behavioral of gowin_multalu27x18;

```

```

        end if;
    end if;
end process;

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            out_reg<=(others=>'0');
        else
            if(ce='1')then
                out_reg<= pp_reg - c_reg;
            end if;
        end if;
    end if;
end process;
dout<=out_reg;
end Behavioral;

```

10.3.2 Dynamic Multiply-add/subtract Examples

Dynamic Multiply-add/subtract with Two Multipliers (Verilog)

```

//Dynamic multiply-add/subtract with 2-bit multiplier
// 1 latency stage on operands
// 2 latency stage after the multiplication
//device: GW5A
module gowin_multaddalu12x12(a0,a1,b0,b1,clk,ce,rst,addsub,dout);
input signed[11:0]a0,a1;
input signed[11:0]b0,b1;
input [1:0]clk,ce,rst;
input[1:0] addsub;
output signed[23:0]dout;
reg signed[11:0]a0_reg,a1_reg;
reg signed[11:0]b0_reg,b1_reg;

reg signed[23:0]p0_reg,p1_reg,dout_reg;

```

```

always@(posedge clk[0])begin
    if (rst[0])begin
        a0_reg<=0;
        b0_reg<=0;
        a1_reg<=0;
        b1_reg<=0;
    end
    else begin
        if(ce[0])begin
            a0_reg<=a0;
            b0_reg<=b0;
            a1_reg<=a1;
            b1_reg<=b1;
        end
    end
end

always@(posedge clk[1])begin
    if (rst[1])begin
        p0_reg<=0;
        p1_reg<=0;
    end
    else begin
        if(ce[1])begin
            p0_reg<=a0_reg*b0_reg;
            p1_reg<=a1_reg*b1_reg;
        end
    end
end

always@(posedge clk[1])begin
    if (rst[1])begin
        dout_reg<=0;
    end
    else begin
        if(ce[1])begin
            dout_reg<= addsub==2'b00 ? p0_reg + p1_reg :

```

```

                                addsub==2'b01 ? p1_reg -p0_reg  :
                                addsub==2'b10 ? p0_reg - p1_reg : -p0_reg-
p1_reg;
                                end
                                end
                                end
                                end

                                assign dout=dout_reg;
                                endmodule

```

Dynamic Multiply-add/subtract with Two Multipliers (VHDL)

```

-- Multiply-add/subtract select with Dynamic control
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity gowin_multaddalu12x12 is
    generic(
        a_width : integer := 11;
        b_width : integer := 11;
        dout_width : integer := 22
    );
    port (
        dout: out unsigned (dout_width-1 downto 0);
        a0,a1 : in unsigned (a_width-1 downto 0);
        b0,b1 : in unsigned (b_width-1 downto 0);
        addsub : in std_logic_vector(1 downto 0);
        clk,ce,rst:in unsigned (1 downto 0)
    );
end gowin_multaddalu12x12;
architecture Behavioral of gowin_multaddalu12x12 is
    signal a0_reg,a1_reg : unsigned (a_width-1 downto 0);
    signal b0_reg,b1_reg : unsigned (b_width-1 downto 0);
    signal p0_reg,p1_reg :unsigned (a_width+b_width-1 downto 0);

```

```
    signal dout_reg :unsigned (dout_width-1 downto 0);
begin
    process(clk(0))begin
        if(rising_edge(clk(0)))then
            if(rst(0)='1')then
                a0_reg<=(others=>'0');
                b0_reg<=(others=>'0');
                a1_reg<=(others=>'0');
                b1_reg<=(others=>'0');
            else
                if(ce(0)='1')then
                    a0_reg<=a0;
                    b0_reg<=b0;
                    a1_reg<=a1;
                    b1_reg<=b1;
                end if;
            end if;
        end if;
    end process;
    process(clk(1))begin
        if(rising_edge(clk(1)))then
            if(rst(1)='1')then
                p0_reg<=(others=>'0');
                p1_reg<=(others=>'0');
            else
                if(ce(1)='1')then
                    p0_reg<=a0_reg*b0_reg;
                    p1_reg<=a1_reg*b1_reg;
                end if;
            end if;
        end if;
    end process;

    process(clk(1))begin
        if(rising_edge(clk(1)))then
```



```

        if(rst(1)=='1')then
            dout_reg<=(others=>'0');
        else
            if(ce(1)=='1')then
                if(addsub="00")then
                    dout_reg <= p0_reg + p1_reg;
                elsif(addsub="01")then
                    dout_reg <= '0'-p0_reg+p1_reg ;
                elsif(addsub="10")then
                    dout_reg <= p0_reg - p1_reg;
                else
                    dout_reg <= '0'-p0_reg - p1_reg;
                end if;
            end if;
        end if;
    end process;
    dout<=dout_reg;
end Behavioral;

```

Dynamic Multiply-add/subtract with Multipliers and Addends (Verilog)

```

// Multiply-add/subtract select with Dynamic control
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW5A
module gowin_multalu27x18 (a,b,c,clk,ce,rst,sel,addsub,out);
    input signed[11:0]a;
    input signed[11:0]b;
    input signed[47:0]c;
    input  [1:0]clk,ce,rst;
    input sel;
    input[1:0] addsub;
    output signed[47:0]out;
    reg signed[11:0]a_reg;
    reg signed[11:0]b_reg;

```

```
reg signed[47:0]c_reg;

reg signed[47:0]pp_reg,out_reg;
wire signed[47:0]c_sig;
assign c_sig=sel ? c_reg : 0;
always@(posedge clk[0])begin
    if (rst[0])begin
        a_reg<=0;
        b_reg<=0;
        c_reg<=0;
    end
    else begin
        if(ce[0])begin
            a_reg<=a;
            b_reg<=b;
            c_reg<=c;
        end
    end
end
always@(posedge clk[1])begin
    if (rst[1])begin
        pp_reg<=0;
    end
    else begin
        if(ce[1])begin
            pp_reg<=a_reg*b_reg;
        end
    end
end
always@(posedge clk[1])begin
    if (rst[1])begin
        out_reg<=0;
    end
    else begin
        if(ce[1])begin
```

```

        out_reg<= addsub==2'b00 ? pp_reg + c_sig :
                    addsub==2'b01 ? -pp_reg + c_sig:
                    addsub==2'b10 ? pp_reg - c_sig : -pp_reg-
c_sig;
    end
end
end

assign out=out_reg;
endmodule

```

Dynamic Multiply-add/subtract with Multipliers and Addends (VHDL)

```

-- Multiply-add/subtract select with Dynamic control
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity gowin_multalu27x18 is
    generic(
        a_width : integer := 12;
        b_width : integer := 12;
        c_width : integer := 48;
        dout_width : integer := 48
    );
    port (
        dout: out signed (dout_width-1 downto 0);
        a : in signed (a_width-1 downto 0);
        b : in signed (b_width-1 downto 0);
        c : in signed (c_width-1 downto 0);
        sel : in std_logic;
        addsub : in std_logic_vector(1 downto 0);
        clk,ce,rst:in signed (1 downto 0)
    );
end gowin_multalu27x18;

```

```

architecture Behavioral of gowin_multalu27x18 is
    signal a_reg : signed (a_width-1 downto 0);
    signal b_reg : signed (b_width-1 downto 0);
    signal c_reg : signed (c_width-1 downto 0);
    signal pp_reg: signed (a_width+b_width-1 downto 0);
    signal c_sig: signed (c_width-1 downto 0);
    signal out_reg : signed (dout_width-1 downto 0);
begin
    process(sel,c_reg)begin
        if(sel='1')then
            c_sig<=c_reg;
        else
            c_sig<=(others=>'0');
        end if;
    end process;

    process(clk(0))begin
        if(rising_edge(clk(0)))then
            if(rst(0)='1')then
                a_reg<=(others=>'0');
                b_reg<=(others=>'0');
                c_reg<=(others=>'0');
            else
                if(ce(0)='1')then
                    a_reg<=a;
                    b_reg<=b;
                    c_reg<=c;
                end if;
            end if;
        end if;
    end process;

    process(clk(1))begin
        if(rising_edge(clk(1)))then
            if(rst(1)='1')then
                pp_reg<=(others=>'0');
            end if;
        end if;
    end process;
end architecture Behavioral of gowin_multalu27x18;

```

```

        else
            if(ce(1)=='1')then
                pp_reg<=a_reg*b_reg;
            end if;
        end if;
    end if;
end process;

process(clk(1))begin
    if(rising_edge(clk(1)))then
        if(rst(1)=='1')then
            out_reg<=(others=>'0');
        else
            if(ce(1)=='1')then
                if(addsub=="00")then
                    out_reg<=pp_reg + c_sig;
                elsif(addsub=="01")then
                    out_reg<= -pp_reg+c_sig ;
                elsif(addsub=="10")then
                    out_reg<= pp_reg - c_sig;
                else
                    out_reg<= -pp_reg - c_sig;
                end if;
            end if;
        end if;
    end if;
end process;

dout<=out_reg;
end Behavioral;

```

10.4 Accumulator

10.4.1 Static Accumulator Examples

$\sum(A*B)$ (Verilog)

// Static accumulation of multiplier($\sum(A*B)$)

```
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW1N/GW2A
module gowin_multalu36x18 (a,b,clk,ce,rst,out);
parameter widtha=26;
parameter widthb=17;

input [widtha-1:0]a;
input [widthb-1:0]b;
input clk,ce,rst;
output [widtha+widthb-1:0]out;
reg [widtha+widthb-1:0]out_reg;
reg [widtha-1:0]a_reg;
reg [widthb-1:0]b_reg;
wire [widtha+widthb-1:0]s_sel;
reg [widtha+widthb-1:0]mout;
always@(posedge clk)begin
    if (rst)begin
        a_reg<=0;
        b_reg<=0;
    end
    else begin
        if(ce)begin
            a_reg<=a;
            b_reg<=b;
        end
    end
end
assign s_sel= out_reg;

always@(posedge clk)begin
    if (rst)begin
        out_reg<=0;
        mout<=0;
    end
end
```

```

        else begin
            if(ce)begin
                mout<=a_reg*b_reg;
                out_reg<=s_sel+mout;
            end
        end
    end
end
assign out=out_reg;
endmodule

```

$\Sigma(A*B)$ (VHDL)

```

-- Static accumulation of unsigned 26x17 bit multiplier ( $\Sigma(A*B)$ )
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

```

```

entity gowin_multalu27x18 is
    generic(
        a_width : integer := 26;
        b_width : integer := 17;
        dout_width : integer := 43
    );
    port (
        dout: out signed (dout_width-1 downto 0);
        a : in signed (a_width-1 downto 0);
        b : in signed (b_width-1 downto 0);
        clk,ce,rst:in std_logic
    );
end gowin_multalu27x18;

architecture Behavioral of gowin_multalu27x18 is
    signal mout :signed (dout_width -1 downto 0);
    signal s_sel :signed (dout_width -1 downto 0);
    signal out_reg :signed (dout_width-1 downto 0);

```

```
    signal a_reg : signed (a_width-1 downto 0);
    signal b_reg : signed (b_width-1 downto 0);
begin

    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                a_reg<=(others=>'0');
                b_reg<=(others=>'0');
            else
                if(ce='1')then
                    a_reg<=a;
                    b_reg<=b;
                end if;
            end if;
        end if;
    end process;

    s_sel<=out_reg;
    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                out_reg<=(others=>'0');
                mout<=(others=>'0');
            else
                if(ce='1')then
                    mout<=a_reg*b_reg;
                    out_reg<=s_sel+mout;
                end if;
            end if;
        end if;
    end process;
    dout<=out_reg;
end Behavioral;
```


$\Sigma(A0*B0 \pm A1*B1)$ (Verilog)

```

// Static accumulation after multiplier summation( $\Sigma(A0*B0+A1*B1)$ )
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW1N/GW2A
module gowin_multaddalu18x18(a0, a1, b0, b1, s, accload, ce, reset,
clk);
    parameter a_width=18;
    parameter b_width=18;
    parameter s_width=54;
    input unsigned [a_width-1:0] a0, a1;
    input unsigned [b_width-1:0] b0, b1;
    input accload, ce, reset, clk;
    output unsigned [s_width-1:0] s;
    wire unsigned [s_width-1:0] s_sel;
    wire unsigned [s_width-1:0] p0, p1;
    reg unsigned [s_width-1:0] p0_reg=0;
    reg unsigned [s_width-1:0] p1_reg=0;
    reg unsigned [s_width-1:0] s=0;
    reg acc_reg0=1'b0;
    reg acc_reg1=1'b0;
    reg unsigned [a_width-1:0] a0_reg, a1_reg;
    reg unsigned [b_width-1:0] b0_reg, b1_reg;

    always @(posedge clk or posedge reset)begin
        if(reset) begin
            a0_reg <= 0;
            a1_reg <= 0;
            b0_reg <= 0;
            b1_reg <= 0;
        end else if(ce) begin
            a0_reg <= a0;
            a1_reg <= a1;
            b0_reg <= b0;
            b1_reg <= b1;

```

```

        end
    end

    assign p0 = a0_reg*b0_reg;
    assign p1 = a1_reg*b1_reg;
    always @(posedge clk or posedge reset)begin
        if(reset) begin
            p0_reg <= 0;
            p1_reg <= 0;
        end else if(ce) begin
            p0_reg <= p0;
            p1_reg <= p1;
        end
    end
end

always @(posedge clk)begin
    acc_reg0 <= accload;
    acc_reg1 <= acc_reg0;
end

assign s_sel = (acc_reg0 == 1) ? s : 0;
always @(posedge clk or posedge reset)begin
    if(reset) begin
        s <= 0;
    end else if(ce) begin
        s <= s_sel + p0_reg + p1_reg;
    end
end
end
endmodule

```

$\Sigma(A0*B0 \pm A1*B1)$ (VHDL)

```

-- Static accumulation after multiplier summation ( $\Sigma(A0*B0-A1*B1)$ )
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

```

```

entity gowin_multaddalu12x12 is
  generic(
    a0_width : integer := 12;
    a1_width : integer := 12;
    b0_width : integer := 12;
    b1_width : integer := 12;
    s_width : integer := 24
  );
  port (
    s: buffer signed(s_width-1 downto 0);
    a0 : in signed(a0_width-1 downto 0);
    a1 : in signed(a0_width-1 downto 0);
    b0 : in signed(b0_width-1 downto 0);
    b1 : in signed(b0_width-1 downto 0);
    accload: in std_logic;
    ce: in std_logic;
    clock: in std_logic;
    reset: in std_logic
  );
end gowin_multaddalu12x12;

architecture Behavioral of gowin_multaddalu12x12 is
  signal p0: signed(a0_width+b0_width-1 downto 0);
  signal p1: signed(a1_width+b1_width-1 downto 0);
  signal p0_reg: signed(s_width-1 downto 0);
  signal p1_reg: signed(s_width-1 downto 0);
  signal p: signed(s_width-1 downto 0);
  signal s_sel: signed(s_width-1 downto 0);
  signal a0_reg : signed(a0_width-1 downto 0);
  signal a1_reg : signed(a0_width-1 downto 0);
  signal b0_reg : signed(b0_width-1 downto 0);
  signal b1_reg : signed(b0_width-1 downto 0);
begin
  p0<=a0_reg*b0_reg;
  p1<=a1_reg*b1_reg;

```

```
process(clock,reset)begin
    if(reset='1')then
        a0_reg<=(others=>'0');
        b0_reg<=(others=>'0');
        a1_reg<=(others=>'0');
        b1_reg<=(others=>'0');
    else
        if(rising_edge(clock))then
            if(ce='1')then
                a0_reg<=a0;
                b0_reg<=b0;
                a1_reg<=a1;
                b1_reg<=b1;
            end if;
        end if;
    end if;
end process;

process(clock,reset)begin
    if(reset='1')then
        p0_reg<=(others=>'0');
        p1_reg<=(others=>'0');
    else
        if(rising_edge(clock))then
            if(ce='1')then
                p0_reg<=resize(p0,s_width);
                p1_reg<=resize(p1,s_width);
            end if;
        end if;
    end if;
end process;

process(accload,s)begin
    if(accload='1')then
        s_sel<=s;
```

```

        else
            s_sel<=(others=>'0');
        end if;
    end process;

    process(clock,reset)begin
        if(reset='1')then
            s<=(others=>'0');
        else
            if(rising_edge(clock))then
                if(ce='1')then
                    s<=s_sel+p0_reg-p1_reg;
                end if;
            end if;
        end if;
    end process;
end Behavioral;

```

10.4.2 Dynamic Accumulator Examples

Dynamic Selection of $\sum(A*B)$ (Verilog)

```

// Accumulation select with Dynamic control( $\sum(A*B)$ )
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW1N/GW2A
module gowin_multalu36x18 (a,b,clk,ce,rst,accsel,out);
parameter PRE_LOAD = 48'h000000000012;
input [25:0]a;
input [16:0]b;
input  clk,ce,rst;
input accsel;
output [42:0]out;
reg [42:0]out_reg;
wire [42:0]s_sel;
reg [42:0]mout;
reg [25:0]a_reg;

```

```

reg [16:0]b_reg;
always@(posedge clk)begin
    if (rst)begin
        a_reg<=0;
        b_reg<=0;
    end
    else begin
        if(ce)begin
            a_reg<=a;
            b_reg<=b;
        end
    end
end

assign s_sel= accsel == 1'b1 ? out_reg : PRE_LOAD;

always@(posedge clk)begin
    if (rst)begin
        out_reg<=0;
        mout<=0;
    end
    else begin
        if(ce)begin
            mout<=a_reg*b_reg;
            out_reg<=s_sel+mout;
        end
    end
end

assign out=out_reg;
endmodule

```

Dynamic Selection of $\sum(A*B)$ (VHDL)

```

-- Accumulation select with Dynamic control( $\sum(A*B)$ )
-- 1 latency stage on operands
-- 2 latency stage after the multiplication

```

```

-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity gowin_multalu27x18 is
  generic(
    a_width : integer := 26;
    b_width : integer := 17;
    dout_width : integer := 43
  );
  port (
    dout: out unsigned (dout_width-1 downto 0);
    a : in unsigned (a_width-1 downto 0);
    b : in unsigned (b_width-1 downto 0);
    accsel : in std_logic;
    clk,ce,rst:in std_logic
  );
end gowin_multalu27x18;

architecture Behavioral of gowin_multalu27x18 is
  signal a_reg :  unsigned (a_width-1 downto 0);
  signal b_reg :  unsigned (b_width-1 downto 0);
  signal mout,s_sel :unsigned (dout_width-1 downto 0);
  signal out_reg :unsigned (dout_width-1 downto 0);
begin
  process(clk)begin
    if(rising_edge(clk))then
      if(rst='1')then
        a_reg<=(others=>'0');
        b_reg<=(others=>'0');
      else
        if(ce='1')then
          a_reg<=a;
          b_reg<=b;
        end if;
      end if;
    end if;
  end process;
end Behavioral;

```

```

        end if;
    end if;
end process;

process(accsel,out_reg)begin
    if(accsel='1')then
        s_sel<=out_reg;
    else
        s_sel<="000"&x"0000000012";
    end if;
end process;

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            out_reg<=(others=>'0');
            mout<=(others=>'0');
        else
            if(ce='1')then
                out_reg<=s_sel + mout;
                mout<=a_reg*b_reg;
            end if;
        end if;
    end if;
end process;

dout<=out_reg;
end Behavioral;

```

Dynamic Selection of $\sum(A0*B0 \pm A1*B1)$ (Verilog)

```

// Accumulation select with Dynamic control( $\sum(A0*B0 \pm A1*B1)$ )
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW5A

module gowin_multaddalu12x12 (a0,a1,b0,b1,clk,addsub,ce, rst,
accsel, dout);

```



```
parameter width=12;
parameter widthout=width*2;
parameter PRE_LOAD = 48'h0000000000012;
input signed[width-1:0]a0,a1;
input signed[width-1:0]b0,b1;
input  [1:0]clk,ce,rst;
input [1:0]addsub;
input accsel;
output signed[widthout:0]dout;
reg signed[width-1:0]a0_reg,a1_reg;
reg signed[width-1:0]b0_reg,b1_reg;
reg signed[widthout:0]out_reg,fb_reg;
reg signed[widthout-1:0]p0_reg,p1_reg;
wire signed[widthout-1:0]mult0,mult1;
wire signed[widthout:0]acc_sel;
wire signed[widthout:0]add_sub;

assign acc_sel = accsel ? fb_reg : PRE_LOAD;
always@(posedge clk[0])begin
    if (rst[0])begin
        a0_reg<=0;
        b0_reg<=0;
        a1_reg<=0;
        b1_reg<=0;
    end
    else begin
        if(ce[0])begin
            a0_reg<=a0;
            b0_reg<=b0;
            a1_reg<=a1;
            b1_reg<=b1;
        end
    end
end
end
```

```

assign mult0=a0_reg*b0_reg;
assign mult1=a1_reg*b1_reg;

```

```

always@(posedge clk[1])begin
    if (rst[1])begin
        p0_reg<=0;
        p1_reg<=0;
    end
    else begin
        if(ce[1])begin
            p0_reg<=mult0;
            p1_reg<=mult1;
        end
    end
end
end

```

```

assign add_sub=addsub==2'b00 ? p0_reg + p1_reg :
            addsub==2'b01 ? -p0_reg +p1_reg:
            addsub==2'b10 ? p0_reg - p1_reg : -p0_reg-
p1_reg;

```

```

always@(posedge clk[1])begin
    if (rst[1])begin
        out_reg<=0;
    end
    else begin
        if(ce[1])begin
            out_reg<=add_sub+acc_sel;
        end
    end
end
end

```

```

always@(posedge clk[1])begin
    if (rst[1])begin
        fb_reg<=0;
    end
end

```

```

        else begin
            if(ce[1])begin
                fb_reg<=out_reg;
            end
        end
    end
end
assign dout=out_reg;
endmodule

```

Dynamic Selection of $\sum(A0*B0 \pm A1*B1)$ (VHDL)

```

-- Accumulation select with Dynamic control( $\sum(A0*B0 \pm A1*B1)$ )
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity gowin_multaddalu12x12 is
    generic(
        a_width : integer := 12;
        b_width : integer := 12;
        dout_width : integer := 24
    );
    port (
        dout: out signed (dout_width-1 downto 0);
        a0,a1 : in signed (a_width-1 downto 0);
        b0,b1 : in signed (b_width-1 downto 0);
        addsub : in std_logic_vector(1 downto 0);
        clk,ce,rst:in signed (1 downto 0)
    );
end gowin_multaddalu12x12;
architecture Behavioral of gowin_multaddalu12x12 is
    signal a0_reg,a1_reg : signed (a_width-1 downto 0);
    signal b0_reg,b1_reg : signed (b_width-1 downto 0);
    signal p0_reg,p1_reg :signed (a_width+b_width-1 downto 0);
    signal fb_reg,dout_reg :signed (dout_width-1 downto 0);

```

```
    signal acc_sel,add_sub :signed (dout_width-1 downto 0);
begin
    acc_sel <= fb_reg;
    process(clk(0))begin
        if(rising_edge(clk(0)))then
            if(rst(0)='1')then
                a0_reg<=(others=>'0');
                b0_reg<=(others=>'0');
                a1_reg<=(others=>'0');
                b1_reg<=(others=>'0');
            else
                if(ce(0)='1')then
                    a0_reg<=a0;
                    b0_reg<=b0;
                    a1_reg<=a1;
                    b1_reg<=b1;
                end if;
            end if;
        end if;
    end process;

    process(clk(1))begin
        if(rising_edge(clk(1)))then
            if(rst(1)='1')then
                p0_reg<=(others=>'0');
                p1_reg<=(others=>'0');
            else
                if(ce(1)='1')then
                    p0_reg<=a0_reg*b0_reg;
                    p1_reg<=a1_reg*b1_reg;
                end if;
            end if;
        end if;
    end process;
    process(addsub,p0_reg , p1_reg)begin
```

```
        if(addsub="00")then
            add_sub <= p0_reg + p1_reg ;
        elsif(addsub="01")then
            add_sub <= '0'-p0_reg+p1_reg ;
        elsif(addsub="10")then
            add_sub <= p0_reg - p1_reg;
        else
            add_sub <= '0'-p0_reg - p1_reg;
        end if;
    end process;

process(clk(1))begin
    if(rising_edge(clk(1)))then
        if(rst(1)='1')then
            dout_reg<=(others=>'0');
        else
            if(ce(1)='1')then
                dout_reg <= add_sub +acc_sel;
            end if;
        end if;
    end if;
end process;

process(clk(1))begin
    if(rising_edge(clk(1)))then
        if(rst(1)='1')then
            fb_reg<=(others=>'0');
        else
            if(ce(1)='1')then
                fb_reg<=dout_reg;
            end if;
        end if;
    end if;
end process;
dout<=dout_reg;
end Behavioral;
```

10.5 Cascadeing

10.5.1 Static Cascadeing Examples

A0*B0±A1*B1±A2*B2±A3*B3 (Verilog)

```
// Static cascade after summing of multipliers (a0*b0+a1*b1+
a2*b2+a3*b3)

// 1 latency stage on operands
// 2 latency stage after the multiplication
//device: GW1N/GW2A

module gowin_multaddalu18x18(a0, a1, a2, b0, b1, b2, a3, b3, s,
clock, ce, reset);
    parameter a_width=18;
    parameter b_width=18;
    parameter s_width=38;
    input signed [a_width-1:0] a0, a1, a2, b0, b1, b2, a3, b3;
    input clock, ce, reset;
    output signed [s_width-1:0] s;
    wire signed [s_width-1:0] p0, p1, p2, p3, s0, s1;
    reg signed [s_width-1:0] p0_reg=0;
    reg signed [s_width-1:0] p1_reg=0;
    reg signed [s_width-1:0] p2_reg=0;
    reg signed [s_width-1:0] p3_reg=0;
    reg signed [s_width-1:0] s0_reg=0;
    reg signed [s_width-1:0] s1_reg=0;
    reg signed [a_width-1:0] a0_reg=18'h00000;
    reg signed [a_width-1:0] a1_reg=18'h00000;
    reg signed [a_width-1:0] a2_reg=18'h00000;
    reg signed [a_width-1:0] a3_reg=18'h00000;
    reg signed [b_width-1:0] b0_reg=18'h00000;
    reg signed [b_width-1:0] b1_reg=18'h00000;
    reg signed [b_width-1:0] b2_reg=18'h00000;
    reg signed [b_width-1:0] b3_reg=18'h00000;
    always @(posedge clock or posedge reset)begin
        if(reset)begin
            a0_reg <= 0;
            a1_reg <= 0;
```

```
        a2_reg <= 0;
        a3_reg <= 0;
        b0_reg <= 0;
        b1_reg <= 0;
        b2_reg <= 0;
        b3_reg <= 0;
    end else begin
        if(ce)begin
            a0_reg <= a0;
            a1_reg <= a1;
            a2_reg <= a2;
            a3_reg <= a3;
            b0_reg <= b0;
            b1_reg <= b1;
            b2_reg <= b2;
            b3_reg <= b3;
        end
    end
end

assign p0 = a0_reg*b0_reg;
assign p1 = a1_reg*b1_reg;
assign p2 = a2_reg*b2_reg;
assign p3 = a3_reg*b3_reg;

always @(posedge clock or posedge reset)begin
    if(reset)begin
        p0_reg <= 0;
        p1_reg <= 0;
        p2_reg <= 0;
        p3_reg <= 0;
    end else begin
        if(ce)begin
            p0_reg <= p0;
            p1_reg <= p1;
```

```

        p2_reg <= p2;
        p3_reg <= p3;
    end
end
end

assign s0 = p0_reg + p1_reg;
always @(posedge clock or posedge reset)begin
    if(reset)begin
        s0_reg <= 0;
    end else begin
        if(ce)begin
            s0_reg <= s0;
        end
    end
end
end
assign s1 = s0_reg + p2_reg + p3_reg;
always @(posedge clock or posedge reset)begin
    if(reset)begin
        s1_reg <= 0;
    end else begin
        if(ce)begin
            s1_reg <= s1;
        end
    end
end
end
assign s=s1_reg;
endmodule

```

$A_0 \cdot B_0 \pm A_1 \cdot B_1 \pm A_2 \cdot B_2 \pm A_3 \cdot B_3$ (VHDL)

-- Static cascade after summing of multipliers($a_0 \cdot b_0 + a_1 \cdot b_1 + d_0 \cdot d_1 + d_2 \cdot d_3$)

-- 1 latency stage on operands

-- 2 latency stage after the multiplication

-- device: GW5A

library IEEE;


```

use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity gowin_top is
    generic(
        a_width : integer := 11;
        b_width : integer := 11;
        dout_width : integer := 23
    );
    port (
        clk,ce,rst: in std_logic;
        mout: out unsigned (dout_width-1 downto 0);
        a,a1,d0,d1 : in unsigned (a_width-1 downto 0);
        b,b1,d2,d3 : in unsigned (b_width-1 downto 0)
    );
end gowin_top;
architecture Behavioral of gowin_top is
    signal mult1,mult2,mult3,mult4:unsigned(dout_width-2 downto 0);
    signal a_reg,a1_reg,d0_reg,d1_reg : unsigned (a_width-1
downto 0);
    signal b_reg,b1_reg,d2_reg,d3_reg : unsigned (b_width-1
downto 0);
    signal p0_reg,p1_reg : unsigned (dout_width-2 downto 0);
begin
    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                a_reg <=(others=>'0');
                a1_reg<=(others=>'0');
                b_reg <=(others=>'0');
                b1_reg<=(others=>'0');
                d0_reg<=(others=>'0');
                d1_reg<=(others=>'0');
                d2_reg<=(others=>'0');
                d3_reg<=(others=>'0');
            else

```

```

        if(ce='1')then
            a_reg <=a;
            a1_reg<=a1;
            b_reg <=b;
            b1_reg<=b1;
            d0_reg<=d0;
            d1_reg<=d1;
            d2_reg<=d2;
            d3_reg<=d3;
        end if;
    end if;
end if;
end process;

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            mout<=(others=>'0');
            p0_reg<=(others=>'0');
            p1_reg<=(others=>'0');
        else
            if(ce='1')then
                mout<=(p0_reg(dout_width-2) & p0_reg) +
(p1_reg(dout_width-2) & p1_reg);
                p0_reg<=a_reg*b_reg + d0_reg*d1_reg;
                p1_reg<=a1_reg*b1_reg + d2_reg*d3_reg;
            end if;
        end if;
    end if;
end process;
end Behavioral;

```

A0*B0±A1*B1 (Verilog)

```

// Static cascading of multipliers( a*b+a1*b1)
// 1 latency stage on operands
// 2 latency stage after the multiplication

```

```
// device: GW1N/GW2A
module gowin_multalu36x18(clk,ce,rst,a,b,a1,b1,dout);
parameter widtha=36;
parameter widthb=18;
parameter widthout=widtha+widthb;
input signed[widtha-1:0]a,a1;
input signed[widthb-1:0]b,b1;
input clk,ce,rst;
output reg signed[widthout-1:0]dout;
reg signed[widtha-1:0]a_reg,a1_reg;
reg signed[widthb-1:0]b_reg,b1_reg;
reg signed[widthout-1:0]p0_reg,p1_reg;

always@(posedge clk)begin
    if(rst)begin
        a_reg <= 0;
        a1_reg <= 0;
        b_reg <= 0;
        b1_reg <= 0;
    end
    else begin
        if(ce)begin
            a_reg <= a;
            a1_reg <= a1;
            b_reg <= b;
            b1_reg <= b1;
        end
    end
end

always@(posedge clk)begin
    if(rst)begin
        p0_reg <= 0;
        p1_reg <= 0;
    end
end
```

```

        else begin
            if(ce)begin
                p0_reg <= a_reg*b_reg;
                p1_reg <= a1_reg*b1_reg;
            end
        end
    end
end

always@(posedge clk)begin
    if(rst)begin
        dout <= 0;
    end
    else begin
        if(ce)begin
            dout<=p0_reg+p1_reg;
        end
    end
end
endmodule

```

A0*B0±A1*B1 (VHDL)

```

-- Static cascading of multipliers(a*b+a1*b1)
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity gowin_multalu27x18 is
    generic(
        a_width : integer := 27;
        b_width : integer := 18;
        dout_width : integer := 46
    );
    port (

```

```

        dout: out signed (dout_width-1 downto 0);
        a,a1 : in signed (a_width-1 downto 0);
        b,b1 : in signed (b_width-1 downto 0);
        clk,ce,rst:in std_logic_vector(1 downto 0)
    );
end gowin_multalu27x18;
architecture Behavioral of gowin_multalu27x18 is
    signal a_reg,a1_reg : signed (a_width-1 downto 0);
    signal b_reg,b1_reg : signed (b_width-1 downto 0);
    signal p0_reg,p1_reg :signed (dout_width -2 downto 0);
begin
    process(clk(0))begin
        if(rising_edge(clk(0)))then
            if(rst(0)='1')then
                a_reg<=(others=>'0');
                a1_reg<=(others=>'0');
                b_reg<=(others=>'0');
                b1_reg<=(others=>'0');
            else
                if(ce(0)='1')then
                    a_reg<=a;
                    a1_reg<=a1;
                    b_reg<=b;
                    b1_reg<=b1;
                end if;
            end if;
        end if;
    end process;

    process(clk(1))begin
        if(rising_edge(clk(1)))then
            if(rst(1)='1')then
                p0_reg<=(others=>'0');
                p1_reg<=(others=>'0');
            else

```

```

        if(ce(1)=='1')then
            p0_reg<=a_reg*b_reg;
            p1_reg<=a1_reg*b1_reg;
        end if;
    end if;
end if;
end process;

process(clk(1))begin
    if(rising_edge(clk(1)))then
        if(rst(1)=='1')then
            dout<=(others=>'0');
        else
            if(ce(1)=='1')then
                dout<=(p0_reg(dout_width-2) & p0_reg) +
(p1_reg(dout_width-2) & p1_reg);
            end if;
        end if;
    end if;
end process;
end Behavioral;

```

10.5.2 Dynamic Cascadeing Examples

Dynamic Selection of $A0*B0 \pm A1*B1$ (Verilog)

```

// Cascade select with Dynamic control(a*b+a1*b1))
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW5A
module gowin_multalu27x18(clk,ce,rst,sel,a,b,a1,b1,out);
    parameter widtha=26;
    parameter widthb=17;
    parameter widthout=widtha+widthb;

    input [widtha-1:0]a,a1;
    input [widthb-1:0]b,b1;
    input clk,ce,rst;

```

```
input sel;
output reg [widthout:0]out;
reg [widtha-1:0]a_reg,a1_reg;
reg [widthb-1:0]b_reg,b1_reg;
reg [widthout-1:0]p0_reg,p1_reg;

always@(posedge clk)begin
    if(rst)begin
        a_reg <= 0;
        a1_reg <= 0;
        b_reg <= 0;
        b1_reg <= 0;
    end
    else begin
        if(ce)begin
            a_reg <= a;
            a1_reg <= a1;
            b_reg <= b;
            b1_reg <= b1;
        end
    end
end

always@(posedge clk)begin
    if(rst)begin
        p0_reg <= 0;
        p1_reg <= 0;
    end
    else begin
        if(ce)begin
            p0_reg <= a_reg*b_reg;
            p1_reg <= a1_reg*b1_reg;
        end
    end
end
```

```

always@(posedge clk)begin
    if(rst)begin
        out <= 0;
    end
    else begin
        if(ce)begin
            out <= sel ? p0_reg + p1_reg : p1_reg;
        end
    end
end
endmodule

```

Dynamic Selection of $A0*B0 \pm A1*B1$ (VHDL)

```

-- Cascade select with Dynamic control( $a*b+a1*b1$ )
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

```

```

entity gowin_top is
    generic(
        a_width : integer := 26;
        b_width : integer := 17;
        dout_width : integer := 43
    );
    port (
        dout: out unsigned (dout_width-1 downto 0);
        a,a1 : in unsigned (a_width-1 downto 0);
        b,b1 : in unsigned (b_width-1 downto 0);
        sel : in std_logic;
        clk,ce,rst:in std_logic
    );
end gowin_top;

```


architecture Behavioral of gowin_top is

```

    signal a_reg,a1_reg : unsigned (a_width-1 downto 0);
    signal b_reg,b1_reg : unsigned (b_width-1 downto 0);
    signal p0_reg,p1_reg :unsigned (dout_width -1 downto 0);

```

begin

```

    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                a_reg<=(others=>'0');
                a1_reg<=(others=>'0');
                b_reg<=(others=>'0');
                b1_reg<=(others=>'0');
            else
                if(ce='1')then
                    a_reg<=a;
                    a1_reg<=a1;
                    b_reg<=b;
                    b1_reg<=b1;
                end if;
            end if;
        end if;
    end process;

```

```

    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                p0_reg<=(others=>'0');
                p1_reg<=(others=>'0');
            else
                if(ce='1')then
                    p0_reg<=a_reg*b_reg;
                    p1_reg<=a1_reg*b1_reg;
                end if;
            end if;
        end if;
    end process;

```

```

end process;

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            dout<=(others=>'0');
        else
            if(ce='1')then
                if(sel='1')then
                    dout<=p0_reg+p1_reg;
                else
                    dout<=p1_reg;
                end if;
            end if;
        end if;
    end if;
end process;
end Behavioral;

```

Dynamic Selection of $A0*B0 \pm A1*B1 \pm A2*B2 \pm A3*B3$ (Verilog)

```

// Cascade select with Dynamic control( $a0*b0 \pm a1*b1 \pm a2*b2 \pm a3*b3$ )
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW5A

module gowin_multaddalu12x12(clk,ce,rst,sel,a0,a1,d0, d1,b0, b1, d2,
d3,dout);
    parameter widtha=12;
    parameter widthb=12;
    parameter widthout=widtha+widthb;

    input signed[widtha-1:0]a0,a1,d0,d1;
    input signed[widthb-1:0]b0,b1,d2,d3;
    input [1:0]clk,ce,rst;
    input sel;
    output reg signed[widthout:0]dout;
    reg signed[widtha-1:0]a0_reg,a1_reg,d0_reg,d1_reg;

```

```

reg signed[widthb-1:0]b0_reg,b1_reg,d2_reg,d3_reg;
reg signed[widthout-1:0]p0_reg,p1_reg,p2_reg,p3_reg;

```

```

always@(posedge clk[0])begin

```

```

    if(rst[0])begin

```

```

        a0_reg <= 0;

```

```

        a1_reg <= 0;

```

```

        b0_reg <= 0;

```

```

        b1_reg <= 0;

```

```

        d0_reg <= 0;

```

```

        d1_reg <= 0;

```

```

        d2_reg <= 0;

```

```

        d3_reg <= 0;

```

```

    end

```

```

    else begin

```

```

        if(ce[0])begin

```

```

            a0_reg <= a0;

```

```

            a1_reg <= a1;

```

```

            b0_reg <= b0;

```

```

            b1_reg <= b1;

```

```

            d0_reg <= d0;

```

```

            d1_reg <= d1;

```

```

            d2_reg <= d2;

```

```

            d3_reg <= d3;

```

```

        end

```

```

    end

```

```

end

```

```

always@(posedge clk[1])begin

```

```

    if(rst[1])begin

```

```

        p0_reg <= 0;

```

```

        p1_reg <= 0;

```

```

    end

```

```

    else begin

```

```

        if(ce[1])begin

```

```

        p0_reg <= a0_reg*b0_reg+a1_reg*b1_reg;
        p1_reg <= d0_reg*d1_reg+d2_reg*d3_reg;
    end
end
end

always@(posedge clk[1])begin
    if(rst[1])begin
        dout <= 0;
    end
    else begin
        if(ce[1])begin
            dout <= sel ? p0_reg + p1_reg : p0_reg ;
        end
    end
end
endmodule

```

Dynamic Selection of $A0*B0 \pm A1*B1 \pm A2*B2 \pm A3*B3$ (VHDL)

```

-- Cascade select with Dynamic control( $a*b \pm a1*b1 \pm d0*d1 \pm d2*d3$ )
-- 1 latency stage on operands
-- 2 latency stage after the multiplication
-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

```

```

entity gowin_multalu27x18 is
    generic(
        a_width : integer := 11;
        b_width : integer := 11;
        dout_width : integer := 23
    );
    port (
        clk,ce,rst,sel: in std_logic;
        mout: out unsigned (dout_width-1 downto 0);
    );
end entity

```

```

        a,a1,d0,d1 : in unsigned (a_width-1 downto 0);
        b,b1,d2,d3 : in unsigned (b_width-1 downto 0)
    );
end gowin_multalu27x18;
architecture Behavioral of gowin_multalu27x18 is
    signal mult1,mult2,mult3,mult4:unsigned(dout_width-2 downto 0);
    signal a_reg,a1_reg,d0_reg,d1_reg : unsigned (a_width-1
downto 0);
    signal b_reg,b1_reg,d2_reg,d3_reg : unsigned (b_width-1
downto 0);
    signal p0_reg,p1_reg : unsigned (dout_width-2 downto 0);
begin
    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                a_reg <=(others=>'0');
                a1_reg<=(others=>'0');
                b_reg <=(others=>'0');
                b1_reg<=(others=>'0');
                d0_reg<=(others=>'0');
                d1_reg<=(others=>'0');
                d2_reg<=(others=>'0');
                d3_reg<=(others=>'0');
            else
                if(ce='1')then
                    a_reg <=a;
                    a1_reg<=a1;
                    b_reg <=b;
                    b1_reg<=b1;
                    d0_reg<=d0;
                    d1_reg<=d1;
                    d2_reg<=d2;
                    d3_reg<=d3;
                end if;
            end if;
        end if;
    end process;
end Behavioral;

```

```

        end if;
    end process;

    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                p0_reg<=(others=>'0');
                p1_reg<=(others=>'0');
            else
                if(ce='1')then
                    p0_reg<=a_reg*b_reg + d0_reg*d1_reg;
                    p1_reg<=a1_reg*b1_reg + d2_reg*d3_reg;
                end if;
            end if;
        end if;
    end process;

    process(clk)begin
        if(rising_edge(clk))then
            if(rst='1')then
                mout<=(others=>'0');
            else
                if(ce='1')then
                    if(sel='1')then
                        mout<=(p0_reg(dout_width-2) & p0_reg) +
(p1_reg(dout_width-2) & p1_reg);
                    else
                        mout<=(p0_reg(dout_width-2) & p0_reg);
                    end if;
                end if;
            end if;
        end if;
    end process;
end Behavioral;

```

10.6 Shifting

10.6.1 Shifting Examples

Pre-adder Followed by shift of Multiplier (Verilog)

```
// Unsigned pre-adder followed by shift of multiplier
// 1 latency stage on operands
// 2 latency stage after the multiplication
// device: GW1N/GW2A
module gowin_padd_mult(a0, a1, b0, b1, p0, p1, clk, ce, reset);
parameter a_width=18;
parameter b_width=18;
parameter p_width=36;
input [a_width-1:0] a0, a1;
input [b_width-1:0] b0, b1;
input clk, ce, reset;
output reg[p_width-1:0] p0, p1;
wire [b_width-1:0] b0_padd, b1_padd;
reg [b_width-1:0] b0_reg=18'h00000;
reg [b_width-1:0] b1_reg=18'h00000;
reg [b_width-1:0] bX1=18'h00000;
reg [b_width-1:0] bY1=18'h00000;
reg[p_width-1:0] p0_reg, p1_reg;
always @(posedge clk or posedge reset)
begin
    if(reset)begin
        b0_reg <= 0;
        b1_reg <= 0;
        bX1 <= 0;
        bY1 <= 0;
    end else begin
        if(ce)begin
            b0_reg <= b0;
            b1_reg <= b1;
            bX1 <= b0_reg;
            bY1 <= b1_reg;
```

```

        end
    end
end
assign b0_padd = bX1 + b1_reg;
assign b1_padd= b0_reg + bY1;

always @(posedge clk or posedge reset)
begin
    if(reset)begin
        p0_reg <= 0;
        p1_reg <= 0;
    end else begin
        if(ce)begin
            p0_reg <= a0 * b0_padd;
            p1_reg <= a1 * b1_padd;
        end
    end
end
always @(posedge clk or posedge reset)
begin
    if(reset)begin
        p0 <= 0;
        p1 <= 0;
    end else begin
        if(ce)begin
            p0<=p0_reg;
            p1<=p1_reg;
        end
    end
end
endmodule

```

Pre-adder Followed by shift of Multiplier (VHDL)

```

-- Unsigned pre-adder followed by shift of multiplier
-- 1 latency stage on operands
-- 2 latency stage after the multiplication

```



```

-- device: GW5A
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity gowin_multalu27x18 is
  generic(
    a_width : integer := 26;
    b_width : integer := 18;
    dout_width : integer := 45
  );
  port (
    p0,p1: out signed (dout_width-1 downto 0);
    a,d0,d1 : in signed (a_width-1 downto 0);
    b0,b1 : in signed (b_width-1 downto 0);
    clk,ce,rst:in std_logic
  );
end gowin_multalu27x18;
architecture Behavioral of gowin_multalu27x18 is
  signal a_reg0,a_reg1 ,a_reg2,d0_reg,d1_reg: signed (a_width-1
downto 0);
  signal paddsub0,paddsub1 :signed (a_width downto 0);
  signal p0_reg,p1_reg:   signed (dout_width-1 downto 0);
begin
  process(clk)begin
    if(rising_edge(clk))then
      if(rst='1')then
        a_reg0<=(others=>'0');
        a_reg1<=(others=>'0');
        a_reg2<=(others=>'0');
        d0_reg<=(others=>'0');
        d1_reg<=(others=>'0');
      else
        if(ce='1')then
          a_reg0<=a;

```

```

        a_reg1<=a_reg0;
        a_reg2<=a_reg1;
        d0_reg<=d0;
        d1_reg<=d1;
    end if;
end if;
end if;
end process;

    paddsub0<=(a_reg0(a_width-1) & a_reg0) + (d0_reg (a_width-1)
& d0_reg);
    paddsub1<=(a_reg2(a_width-1) & a_reg2) + (d1_reg (a_width-1)
& d1_reg);

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            p0_reg<=(others=>'0');
            p1_reg<=(others=>'0');
        else
            if(ce='1')then
                p0_reg<=paddsub0 * b0;
                p1_reg<=paddsub1 * b1;
            end if;
        end if;
    end if;
end process;

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            p0<=(others=>'0');
            p1<=(others=>'0');
        else
            if(ce='1')then

```

```

        p0<=p0_reg;
        p1<=p1_reg;
    end if;
end if;
end if;
end process;

```

```

end Behavioral;

```

10.7 Arithmetic Logic Operation

10.7.1 Arithmetic Logic Examples

48-bit Addition (Verilog)

```

// 48-bit wide addition operation.
// 1 latency stage on operands
// 1 latency stage after the sum
// device: GW1N/GW2A
module gowin_alu54d(a, b, dout, clk, ce, reset);
parameter width=48;
input [width-1:0] a, b;
input clk, ce, reset;
output reg [width-1:0] dout;
wire [width-1:0] s_sel;
reg [width-1:0] a_reg;
reg [width-1:0] b_reg;

always @(posedge clk or posedge reset)
begin
    if(reset)begin
        a_reg <= 0;
        b_reg <= 0;
    end else begin
        if(ce)begin
            a_reg <= a;
            b_reg <= b;
        end
    end
end

```

```

        end
    end

    always @(posedge clk or posedge reset)
    begin
        if(reset)begin
            dout <= 0;
        end else begin
            if(ce)begin
                dout <= a_reg + b_reg;
            end
        end
    end
end
endmodule

```

48-bit Subtraction (VHDL)

```

-- 48-bit subtraction
-- 1 latency stage on operands
-- 1 latency stage after the sum
-- device: GW1N/GW2A
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity gowin_alu54d is
    generic(
        b_width: integer := 48;
        a_width : integer := 48;
        dout_width : integer := 48
    );
    port (
        dout: out std_logic_vector(dout_width-1 downto 0);
        a: in std_logic_vector(a_width-1 downto 0);
        b: in std_logic_vector(b_width-1 downto 0);
        ce: in std_logic;
        clk: in std_logic;
    );
end entity gowin_alu54d;

```

```

        reset: in std_logic
    );
end gowin_alu54d;
architecture Behavioral of gowin_alu54d is
    signal a_reg: std_logic_vector(a_width-1 downto 0);
    signal b_reg: std_logic_vector(b_width-1 downto 0);
begin
    process(clk,reset)begin
        if(reset='1')then
            a_reg<=(others=>'0');
            b_reg<=(others=>'0');
        else
            if(rising_edge(clk))then
                if(ce='1')then
                    a_reg<=a;
                    b_reg<=b;
                end if;
            end if;
        end if;
    end process;

    process(clk,reset)begin
        if(reset='1')then
            dout<=(others=>'0');
        else
            if(rising_edge(clk))then
                if(ce='1')then
                    dout<=a_reg - b_reg;
                end if;
            end if;
        end if;
    end process;
end Behavioral;

```

11_{FSM}

11.1 FSM Description

GowinSynthesis supports Finite State Machine (FSM) specifications in both Moore and Mealy forms. An FSM consists of the following components:

- State register
- Next-state function
- Output function

Moore-type FSM: Outputs depend solely on the current state (independent of input changes).

Mealy-type FSM: Outputs depend on both the current state and input signals.

11.2 Encoding Schemes

- One-hot encoding: Each state is represented by a dedicated flip-flop. For an FSM with N states, N bits are used, where each state corresponds to one bit being "1" and all others "0".
- Gray code encoding: Only one bit changes between adjacent states.
- Sequential encoding: Uses the minimum number of bits ($\log_2(N)$) to represent N states, with states encoded in binary sequence.

11.3 FSM Examples

11.3.1 Moore FSM with One-hot Encoding (Verilog)

```
// State Machine with One-hot encoding
module gowin_fsm (clk,rst,sel,qout);
input clk;
input rst;
input [1:0]sel;
output reg [7:0] qout;
```

```
localparam S0 = 6'b00_0001;
localparam S1 = 6'b00_0010;
localparam S2 = 6'b00_0100;
localparam S3 = 6'b00_1000;
localparam S4 = 6'b01_0000;
localparam S5 = 6'b10_0000;

reg [5:0] curr_state;
reg [5:0] next_state;
always @(posedge clk or posedge rst) begin
    if(rst)
        curr_state <= S0;
    else
        curr_state <= next_state;
end

always @(*) begin
    next_state = S0;
    case(curr_state)
        S0 :begin
            if(sel == 2'b00)
                next_state = S1;
            else
                next_state = S0;
            end
        S1 :begin
            if(sel == 2'b01)
                next_state = S2;
            else
                next_state = S1;
            end
        S2 :begin
            if(sel == 2'b10)
```

```
        next_state = S3;
    else
        next_state = S2;
    end

S3 :begin
    if(sel == 2'b11)
        next_state = S4;
    else
        next_state = S3;
    end
S4 :begin
    if(sel == 2'b00)
        next_state = S4;
    else
        next_state = S5;
    end
S5 :begin
    if(sel == 2'b01)
        next_state = S5;
    else
        next_state = S0;
    end
    default:next_state = S0;
endcase
end
always @(posedge clk or posedge rst) begin
    if(rst) begin
        qout <= 0;
    end
    else begin
        if(curr_state==S5)begin
            qout <= 8'h10;
        end
    end
end
```



```
end  
endmodule
```

11.3.2 Moore FSM with One-hot Encoding (VHDL)

```
-- State Machine with One-hot encoding  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
  
entity gowin_fsm is  
    port(  
        clk : in std_logic;  
        rst : in std_logic;  
        sel : in std_logic_vector(1 downto 0);  
        qout: out std_logic_vector(7 downto 0)  
    );  
end entity;  
  
architecture rtl of gowin_fsm is  
    signal curr_state:std_logic_vector(5 downto 0);  
    signal next_state:std_logic_vector(5 downto 0);  
    constant S0 : std_logic_vector := "000001";  
    constant S1 : std_logic_vector := "000010";  
    constant S2 : std_logic_vector := "000100";  
    constant S3 : std_logic_vector := "001000";  
    constant S4 : std_logic_vector := "010000";  
    constant S5 : std_logic_vector := "100000";  
begin  
    process(clk,rst)begin  
        if(rst='1')then  
            curr_state<=S0;  
        else  
            if(rising_edge(clk))then  
                curr_state<=next_state;  
            end if;  
        end if;  
    end process;  
end architecture;
```

```
        end if;
    end process;

    process(sel,curr_state)begin
        next_state <= S0;
        case curr_state is
            when S0 =>
                if(sel ="00")then
                    next_state <= S1;
                else
                    next_state <= S0;
                end if;
            when S1 =>
                if(sel ="01")then
                    next_state <= S2;
                else
                    next_state <= S1;
                end if;
            when S2 =>
                if(sel ="10")then
                    next_state <= S3;
                else
                    next_state <= S2;
                end if;
            when S3 =>
                if(sel ="11")then
                    next_state <= S4;
                else
                    next_state <= S3;
                end if;
            when S4 =>
                if(sel ="00")then
                    next_state <= S4;
                else
```

```

        next_state <= S5;
    end if;
    when S5 =>
        if(sel ="01")then
            next_state <= S5;
        else
            next_state <= S0;
        end if;
    when others=>next_state <= S0;
end case;
end process;

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            qout<=(others=>'0');
        else
            if(curr_state =S5)then
                qout <= "00010000";
            end if;
        end if;
    end if;
end process;
end rtl;

```

11.3.3 Mealy FSM with One-hot Encoding (Verilog)

```

// State Machine with One-hot encoding
module gowin_fsm (clk,rst,sel,din,qout);
    input clk;
    input rst;
    input [1:0]sel;
    input [7:0] din;
    output reg [7:0] qout;
    localparam S0 = 6'b00_0001;
    localparam S1 = 6'b00_0010;

```

```
localparam S2 = 6'b00_0100;
localparam S3 = 6'b00_1000;
localparam S4 = 6'b01_0000;
localparam S5 = 6'b10_0000;

reg [5:0] curr_state;
reg [5:0] next_state;
always @(posedge clk or posedge rst) begin
    if(rst)
        curr_state <= S0;
    else
        curr_state <= next_state;
end

always @(*) begin
    next_state = S0;
    case(curr_state)
        S0 :begin
            if(sel == 2'b00)
                next_state = S1;
            else
                next_state = S0;
        end

        S1 :begin
            if(sel == 2'b01)
                next_state = S2;
            else
                next_state = S1;
        end

        S2 :begin
            if(sel == 2'b10)
                next_state = S3;
            else
```

```
        next_state = S2;
    end

    S3 :begin
        if(sel == 2'b11)
            next_state = S4;
        else
            next_state = S3;
        end
    S4 :begin
        if(sel == 2'b00)
            next_state = S4;
        else
            next_state = S5;
        end
    S5 :begin
        if(sel == 2'b01)
            next_state = S5;
        else
            next_state = S0;
        end
        default:next_state = S0;
    endcase
end
always @(posedge clk or posedge rst) begin
    if(rst) begin
        qout <= 0;
    end
    else begin
        if(curr_state==S5)begin
            qout <= din;
        end
        else begin
            qout <= 8'h10;
        end
    end
end
```

```

        end
    end

endmodule

```

11.3.4 Mealy FSM with One-hot Encoding (VHDL)

```

-- State Machine with One-hot encoding
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity gowin_fsm is
    port(
        clk : in std_logic;
        rst : in std_logic;
        sel : in std_logic_vector(1 downto 0);
        din : in std_logic_vector(7 downto 0);
        qout: out std_logic_vector(7 downto 0)
    );
end entity;

architecture rtl of gowin_fsm is
    signal curr_state:std_logic_vector(5 downto 0);
    signal next_state:std_logic_vector(5 downto 0);
    constant S0 : std_logic_vector := "000001";
    constant S1 : std_logic_vector := "000010";
    constant S2 : std_logic_vector := "000100";
    constant S3 : std_logic_vector := "001000";
    constant S4 : std_logic_vector := "010000";
    constant S5 : std_logic_vector := "100000";
begin
    process(clk,rst)begin
        if(rst='1')then
            curr_state<=S0;
        else

```

```
        if(rising_edge(clk))then
            curr_state<=next_state;
        end if;
    end if;
end process;
```

```
process(sel,curr_state)begin
    next_state <= S0;
    case curr_state is
        when S0 =>
            if(sel ="00")then
                next_state <= S1;
            else
                next_state <= S0;
            end if;
        when S1 =>
            if(sel ="01")then
                next_state <= S2;
            else
                next_state <= S1;
            end if;
        when S2 =>
            if(sel ="10")then
                next_state <= S3;
            else
                next_state <= S2;
            end if;
        when S3 =>
            if(sel ="11")then
                next_state <= S4;
            else
                next_state <= S3;
            end if;
        when S4 =>
```

```

        if(sel ="00")then
            next_state <= S4;
        else
            next_state <= S5;
        end if;
    when S5 =>
        if(sel ="01")then
            next_state <= S5;
        else
            next_state <= S0;
        end if;
    when others=>next_state <= S0;
end case;
end process;

```

```

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            qout<=(others=>'0');
        else
            if(curr_state =S5)then
                qout <=din;
            else
                qout <= "00010000";
            end if;
        end if;
    end if;
end process;
end rtl;

```

11.3.5 Moore FSM with Gray Code Encoding (Verilog)

```

// State Machine with Gray code encoding
module gowin_fsm (clk,rst,sel,qout);
    input clk;
    input rst;

```



```
input [1:0]sel;
output reg [7:0] qout;
localparam S0 = 3'b000;
localparam S1 = 3'b001;
localparam S2 = 3'b011;
localparam S3 = 3'b010;
localparam S4 = 3'b110;
localparam S5 = 3'b111;

reg [2:0] curr_state;
reg [2:0] next_state;
always @(posedge clk or posedge rst) begin
    if(rst)
        curr_state <= S0;
    else
        curr_state <= next_state;
end

always @(*) begin
    next_state = S0;
    case(curr_state)
        S0 :begin
            if(sel == 2'b00)
                next_state = S1;
            else
                next_state = S0;
            end

        S1 :begin
            if(sel == 2'b01)
                next_state = S2;
            else
                next_state = S1;
            end
    end
```

```
S2 :begin
    if(sel == 2'b10)
        next_state = S3;
    else
        next_state = S2;
    end

S3 :begin
    if(sel == 2'b11)
        next_state = S4;
    else
        next_state = S3;
    end

S4 :begin
    if(sel == 2'b00)
        next_state = S4;
    else
        next_state = S5;
    end

S5 :begin
    if(sel == 2'b01)
        next_state = S5;
    else
        next_state = S0;
    end

    default:next_state = S0;
endcase
end

always @(posedge clk or posedge rst) begin
    if(rst) begin
        qout <= 0;
    end
    else begin
        if(curr_state==S5)begin
            qout <= 8'h10;
        end
    end
end
```

```

        end
    end
end

```

```

endmodule

```

11.3.6 Moore FSM with Gray Code Encoding (VHDL)

```

-- State Machine with Gray code encoding
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity gowin_fsm is
    port(
        clk : in std_logic;
        rst : in std_logic;
        sel : in std_logic_vector(1 downto 0);
        qout: out std_logic_vector(7 downto 0)
    );
end entity;

architecture rtl of gowin_fsm is
    signal curr_state:std_logic_vector(2 downto 0);
    signal next_state:std_logic_vector(2 downto 0);
    constant S0 : std_logic_vector := "000";
    constant S1 : std_logic_vector := "001";
    constant S2 : std_logic_vector := "011";
    constant S3 : std_logic_vector := "010";
    constant S4 : std_logic_vector := "110";
    constant S5 : std_logic_vector := "111";
begin
    process(clk,rst)begin
        if(rst='1')then
            curr_state<=S0;
        else

```

```
        if(rising_edge(clk))then
            curr_state<=next_state;
        end if;
    end if;
end process;

process(sel,curr_state)begin
    next_state <= S0;
    case curr_state is
        when S0 =>
            if(sel ="00")then
                next_state <= S1;
            else
                next_state <= S0;
            end if;
        when S1 =>
            if(sel ="01")then
                next_state <= S2;
            else
                next_state <= S1;
            end if;
        when S2 =>
            if(sel ="10")then
                next_state <= S3;
            else
                next_state <= S2;
            end if;
        when S3 =>
            if(sel ="11")then
                next_state <= S4;
            else
                next_state <= S3;
            end if;
        when S4 =>
            if(sel ="00")then
```

```

        next_state <= S4;
    else
        next_state <= S5;
    end if;
when S5 =>
    if(sel ="01")then
        next_state <= S5;
    else
        next_state <= S0;
    end if;
    when others=>next_state <= S0;
end case;
end process;

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            qout<=(others=>'0');
        else
            if(curr_state =S5)then
                qout <= "00010000";
            end if;
        end if;
    end if;
end process;
end rtl;

```

11.3.7 Mealy FSM with Gray Code Encoding (Verilog)

```

// State Machine with Gray code encoding
module gowin_fsm (clk,rst,sel,din,qout);
    input clk;
    input rst;
    input [1:0]sel;
    input [7:0] din;
    output reg [7:0] qout;

```

```
localparam S0 = 3'b000;
localparam S1 = 3'b001;
localparam S2 = 3'b011;
localparam S3 = 3'b010;
localparam S4 = 3'b110;
localparam S5 = 3'b111;
reg [2:0] curr_state;
reg [2:0] next_state;
always @(posedge clk or posedge rst) begin
    if(rst)
        curr_state <= S0;
    else
        curr_state <= next_state;
end

always @(*) begin
    next_state = S0;
    case(curr_state)
        S0 :begin
            if(sel == 2'b00)
                next_state = S1;
            else
                next_state = S0;
        end

        S1 :begin
            if(sel == 2'b01)
                next_state = S2;
            else
                next_state = S1;
        end

        S2 :begin
            if(sel == 2'b10)
                next_state = S3;
```

```
        else
            next_state = S2;
        end

S3 :begin
    if(sel == 2'b11)
        next_state = S4;
    else
        next_state = S3;
    end
S4 :begin
    if(sel == 2'b00)
        next_state = S4;
    else
        next_state = S5;
    end
S5 :begin
    if(sel == 2'b01)
        next_state = S5;
    else
        next_state = S0;
    end
    default:next_state = S0;
endcase
end
always @(posedge clk or posedge rst) begin
    if(rst) begin
        qout <= 0;
    end
    else begin
        if(curr_state==S5)begin
            qout <= din;
        end
        else begin
            qout <= 8'h10;
```

```
        end
    end
end

endmodule
```

11.3.8 Mealy FSM with Gray Code Encoding (VHDL)

```
-- State Machine with Gray code encoding
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity gowin_fsm is
    port(
        clk : in std_logic;
        rst : in std_logic;
        sel : in std_logic_vector(1 downto 0);
        din : in std_logic_vector(7 downto 0);
        qout: out std_logic_vector(7 downto 0)
    );
end entity;

architecture rtl of gowin_fsm is
    signal curr_state:std_logic_vector(2 downto 0);
    signal next_state:std_logic_vector(2 downto 0);
    constant S0 : std_logic_vector := "000";
    constant S1 : std_logic_vector := "001";
    constant S2 : std_logic_vector := "011";
    constant S3 : std_logic_vector := "010";
    constant S4 : std_logic_vector := "110";
    constant S5 : std_logic_vector := "111";
begin
    process(clk,rst)begin
        if(rst='1')then
            curr_state<=S0;
```



```
    else
        if(rising_edge(clk))then
            curr_state<=next_state;
        end if;
    end if;
end process;
```

```
process(sel,curr_state)begin
    next_state <= S0;
    case curr_state is
        when S0 =>
            if(sel ="00")then
                next_state <= S1;
            else
                next_state <= S0;
            end if;
        when S1 =>
            if(sel ="01")then
                next_state <= S2;
            else
                next_state <= S1;
            end if;
        when S2 =>
            if(sel ="10")then
                next_state <= S3;
            else
                next_state <= S2;
            end if;
        when S3 =>
            if(sel ="11")then
                next_state <= S4;
            else
                next_state <= S3;
            end if;
    end case;
end process;
```

```

        when S4 =>
            if(sel ="00")then
                next_state <= S4;
            else
                next_state <= S5;
            end if;
        when S5 =>
            if(sel ="01")then
                next_state <= S5;
            else
                next_state <= S0;
            end if;
        when others=>next_state <= S0;
    end case;
end process;

```

```

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            qout<=(others=>'0');
        else
            if(curr_state =S5)then
                qout <=din;
            else
                qout <= "00010000";
            end if;
        end if;
    end if;
end process;
end rtl;

```

11.3.9 Moore FSM with Sequential Encoding (Verilog)

```

// State Machine with sequential code encoding
module gowin_fsm (clk,rst,sel,qout);
    input clk;

```

```
input rst;
input [1:0]sel;
output reg [7:0] qout;
localparam S0 = 3'b000;
localparam S1 = 3'b001;
localparam S2 = 3'b010;
localparam S3 = 3'b011;
localparam S4 = 3'b100;
localparam S5 = 3'b101;

reg [2:0] curr_state;
reg [2:0] next_state;
always @(posedge clk or posedge rst) begin
    if(rst)
        curr_state <= S0;
    else
        curr_state <= next_state;
end

always @(*) begin
    next_state = S0;
    case(curr_state)
        S0 :begin
            if(sel == 2'b00)
                next_state = S1;
            else
                next_state = S0;
            end

        S1 :begin
            if(sel == 2'b01)
                next_state = S2;
            else
                next_state = S1;
            end
        end
    end
```

```
S2 :begin
    if(sel == 2'b10)
        next_state = S3;
    else
        next_state = S2;
    end

S3 :begin
    if(sel == 2'b11)
        next_state = S4;
    else
        next_state = S3;
    end

S4 :begin
    if(sel == 2'b00)
        next_state = S4;
    else
        next_state = S5;
    end

S5 :begin
    if(sel == 2'b01)
        next_state = S5;
    else
        next_state = S0;
    end

    default:next_state = S0;
endcase
end

always @(posedge clk or posedge rst) begin
    if(rst) begin
        qout <= 0;
    end
    else begin
        if(curr_state==S5)begin
```

```

        qout <= 8'h10;
    end
end
end

```

```

endmodule

```

11.3.10 Moore FSM with Sequential Encoding (VHDL)

```

-- State Machine with sequential code encoding

```

```

library ieee;

```

```

use ieee.std_logic_1164.all;

```

```

use ieee.std_logic_unsigned.all;

```

```

entity gowin_fsm is

```

```

    port(

```

```

        clk : in std_logic;

```

```

        rst : in std_logic;

```

```

        sel : in std_logic_vector(1 downto 0);

```

```

        qout: out std_logic_vector(7 downto 0)

```

```

    );

```

```

end entity;

```

```

architecture rtl of gowin__fsm is

```

```

    signal curr_state:std_logic_vector(2 downto 0);

```

```

    signal next_state:std_logic_vector(2 downto 0);

```

```

    constant S0 : std_logic_vector := "000";

```

```

    constant S1 : std_logic_vector := "001";

```

```

    constant S2 : std_logic_vector := "010";

```

```

    constant S3 : std_logic_vector := "011";

```

```

    constant S4 : std_logic_vector := "100";

```

```

    constant S5 : std_logic_vector := "101";

```

```

begin

```

```

    process(clk,rst)begin

```

```

        if(rst='1')then

```

```

            curr_state<=S0;

```

```
        else
            if(rising_edge(clk))then
                curr_state<=next_state;
            end if;
        end if;
    end process;
```

```
process(sel,curr_state)begin
    next_state <= S0;
    case curr_state is
        when S0 =>
            if(sel ="00")then
                next_state <= S1;
            else
                next_state <= S0;
            end if;
        when S1 =>
            if(sel ="01")then
                next_state <= S2;
            else
                next_state <= S1;
            end if;
        when S2 =>
            if(sel ="10")then
                next_state <= S3;
            else
                next_state <= S2;
            end if;
        when S3 =>
            if(sel ="11")then
                next_state <= S4;
            else
                next_state <= S3;
            end if;
    end case;
end process;
```

```

        when S4 =>
            if(sel ="00")then
                next_state <= S4;
            else
                next_state <= S5;
            end if;
        when S5 =>
            if(sel ="01")then
                next_state <= S5;
            else
                next_state <= S0;
            end if;
        when others=>next_state <= S0;
    end case;
end process;

```

```

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            qout<=(others=>'0');
        else
            if(curr_state =S5)then
                qout <= "00010000";
            end if;
        end if;
    end if;
end process;
end rtl;

```

11.3.11 Mealy FSM with Sequential Encoding (Verilog)

```

// State Machine with sequential code encoding
module gowin_fsm (clk,rst,sel,din,qout);
    input clk;
    input rst;
    input [1:0]sel;

```

```
input [7:0] din;
output reg [7:0] qout;
localparam S0 = 3'b000;
localparam S1 = 3'b001;
localparam S2 = 3'b010;
localparam S3 = 3'b011;
localparam S4 = 3'b100;
localparam S5 = 3'b101;

reg [2:0] curr_state;
reg [2:0] next_state;
always @(posedge clk or posedge rst) begin
    if(rst)
        curr_state <= S0;
    else
        curr_state <= next_state;
end

always @(*) begin
    next_state = S0;
    case(curr_state)
        S0 :begin
            if(sel == 2'b00)
                next_state = S1;
            else
                next_state = S0;
            end

        S1 :begin
            if(sel == 2'b01)
                next_state = S2;
            else
                next_state = S1;
            end
    end
```



```
S2 :begin
    if(sel == 2'b10)
        next_state = S3;
    else
        next_state = S2;
    end

S3 :begin
    if(sel == 2'b11)
        next_state = S4;
    else
        next_state = S3;
    end

S4 :begin
    if(sel == 2'b00)
        next_state = S4;
    else
        next_state = S5;
    end

S5 :begin
    if(sel == 2'b01)
        next_state = S5;
    else
        next_state = S0;
    end

    default:next_state = S0;
endcase
end

always @(posedge clk or posedge rst) begin
    if(rst) begin
        qout <= 0;
    end
    else begin
        if(curr_state==S5)begin
            qout <= din;
        end
    end
end
```

```

        end
    else begin
        qout <= 8'h10;
    end
end
end
endmodule

```

11.3.12 Mealy FSM with Sequential Encoding (VHDL)

```

-- State Machine with sequential code encoding
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity gowin_fsm is
    port(
        clk : in std_logic;
        rst : in std_logic;
        sel : in std_logic_vector(1 downto 0);
        din : in std_logic_vector(7 downto 0);
        qout: out std_logic_vector(7 downto 0)
    );
end entity;

architecture rtl of gowin_fsm is
    signal curr_state:std_logic_vector(2 downto 0);
    signal next_state:std_logic_vector(2 downto 0);
    constant S0 : std_logic_vector := "000";
    constant S1 : std_logic_vector := "001";
    constant S2 : std_logic_vector := "010";
    constant S3 : std_logic_vector := "011";
    constant S4 : std_logic_vector := "100";
    constant S5 : std_logic_vector := "101";
begin

```

```
process(clk,rst)begin
    if(rst='1')then
        curr_state<=S0;
    else
        if(rising_edge(clk))then
            curr_state<=next_state;
        end if;
    end if;
end process;
```

```
process(sel,curr_state)begin
    next_state <= S0;
    case curr_state is
        when S0 =>
            if(sel ="00")then
                next_state <= S1;
            else
                next_state <= S0;
            end if;
        when S1 =>
            if(sel ="01")then
                next_state <= S2;
            else
                next_state <= S1;
            end if;
        when S2 =>
            if(sel ="10")then
                next_state <= S3;
            else
                next_state <= S2;
            end if;
        when S3 =>
            if(sel ="11")then
                next_state <= S4;
```

```
        else
            next_state <= S3;
        end if;
    when S4 =>
        if(sel ="00")then
            next_state <= S4;
        else
            next_state <= S5;
        end if;
    when S5 =>
        if(sel ="01")then
            next_state <= S5;
        else
            next_state <= S0;
        end if;
    when others=>next_state <= S0;
end case;
end process;

process(clk)begin
    if(rising_edge(clk))then
        if(rst='1')then
            qout<=(others=>'0');
        else
            if(curr_state =S5)then
                qout <=din;
            else
                qout <= "00010000";
            end if;
        end if;
    end if;
end if;
end process;
end rtl;
```

